

Current Electricity

Electric current  $\rightarrow$  rate of flow of charge.

Electric current - time interval

$$\text{Inst. } I_{\text{inst.}} = \frac{\Delta q}{\Delta t} \text{ ampere (A)}$$

$$(1 \text{ A} = \frac{1 \text{ C}}{1 \text{ sec}})$$

) Instantaneous electric current  $I = \lim_{\Delta t \rightarrow 0} \left( \frac{\Delta q}{\Delta t} \right)$   
 (current at any instant)

$$I = \frac{dq}{dt}$$

$$dq = I dt$$

$$I = f(t) \quad \text{variable current}$$


Total Charge

$$q = \int_0^t I dt$$

avg current

$$I_{av} = \frac{q}{t}$$

$$\frac{\int I \cdot dt}{t}$$

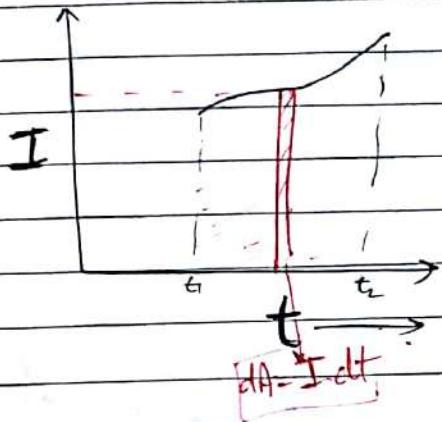
i-t graph

total area under curve.

$$Q = \int_{t_1}^{t_2} I \cdot dt = \text{total charge.}$$

dir of current

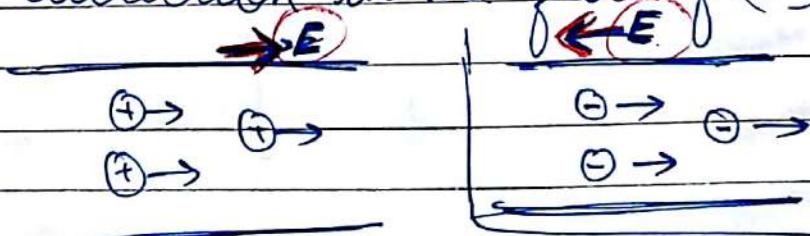It is the direction in the flow of (+ve) charge




not wacent in the right direction

- 1) Conductor free e<sup>-</sup>
- 2) Insulator don't conduct electricity (no free e<sup>-</sup>)
- 3) Semi conductor\*\*

### Current density ( $\vec{J}$ )

It is a vector quantity.

- current per unit normal area

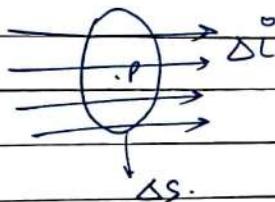

average current density

$$\vec{J}_{\text{avg}} = \frac{\Delta i}{\Delta s}$$


current density at point P

$$\vec{J} = \lim_{\Delta s \rightarrow 0} \left( \frac{\Delta i}{\Delta s} \right)$$

$$\boxed{\vec{J} = \frac{di}{ds}}$$

dir of current density in the dir of current

$$\text{Unit} = \frac{A}{m^2}$$

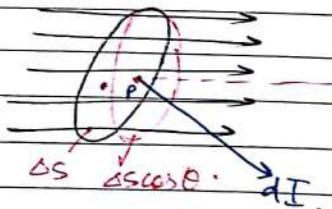

$$I = \frac{\Delta i}{\Delta s \cos \theta}$$

current density  $J$


$$J = \frac{di}{ds \cos \theta}$$

$$di = J \cdot ds \cos \theta$$

$$di = \vec{J} \cdot \vec{ds}$$

net current


$$I = \int \vec{J} \cdot \vec{ds}$$

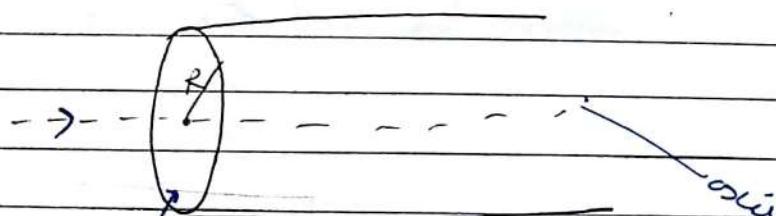

current density  $= J_0 \cdot \text{const}$

$$\text{Current } I = J_0 \cdot (\pi R^2)$$

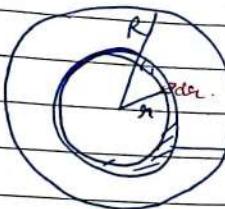(B) current density  $J = J_0 r \leftarrow$  (dis from axis)



$$\text{elemental area } d\sigma' = 2\pi r dr.$$

$$dI = (J_0 r)(2\pi r dr)$$

$$= 2\pi J_0 r^2 dr.$$


net current

$$I = \int_0^R dI.$$

$$= \int_0^R 2\pi r^2 dr J_0 = 2\pi J_0 \cdot \frac{R^3}{3}$$

Relation b/w current (I) and velocity of charged particle

Stream of charged particles

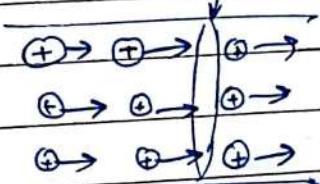

$q \rightarrow$  charge of each particle.

$A \rightarrow$  area of cross section

$v \rightarrow$  velo of particle

$n \rightarrow$  no of charged particles per unit volume.

Current ( $I$ ) = Charge flown through cross section in 1 sec.

$$I = A V n q$$

Aico Velo number charge  
 of each particle

(A)  $\rightarrow V$   
 n v

$$\text{Current density } J = \frac{I}{A} = A V n q$$

Ours  $\rightarrow$  Current flowing in a conductor depends on time ( $t$ ) as  $I = 2t + 3$  A per sec

1) find charge flown through any cross-section from  $t=0$  to  $t=4$  sec

2) Avg current in  $t=0$  to  $t=4$  sec

total charge

$$1) q = \int_0^4 I dt = \int_0^4 (2t+3) dt$$

$$q = 28 \text{ C}$$

$$2) \text{ Avg Current} = \frac{q}{t} = \frac{28}{4} = 7 \text{ A}$$

Q - Calculate no of free e<sup>-</sup> per unit volume in a metallic conductor of density  $10^4 \text{ kg/m}^3$  and mass no = 100 (molecular mass) each atom contributes 1 e<sup>-</sup> free electron.

$$\frac{T}{A} = 10^4 \text{ A}$$

$$10^4 \text{ A} = A v n q$$

$$M_w = 100 \quad d = 10^4 \text{ kg/m}^3$$

$$\begin{aligned} M_w &\longrightarrow N_A \\ (m) &\longrightarrow \frac{N_A}{M_w} \times m \\ (m = v) & \end{aligned}$$

= no of atom per unit vol.

$$= \frac{N_A M}{M_w V}$$

$$\frac{d \cdot N_A}{M_w}$$

$$\text{no of } e^- \text{ per unit vol} = \frac{6.02 \times 10^{23} \times 10^4}{100 \times 10^{-3} (\text{kg})}$$

$$4 \int (at + 3) dt$$

$$0.0 \quad \left( \frac{at^2}{2} + 3t \right)$$

$$\int_0^{at+3} t$$

$$16 + 12$$

$$t^2 + 3t$$


$$16 + 12$$

$$\frac{28}{4} +$$

gravitation  $\rightarrow$  Discuss EX-1 Comp part II.

Current-  
Read

Movement of free- inside conductor

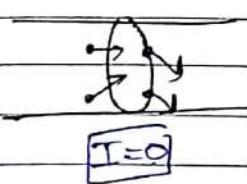

Motion of e<sup>-</sup> → random


$$\langle \vec{v} \rangle = 0$$

$$\langle \vec{v} \rangle = \vec{V}_1 + \vec{V}_2 + \vec{V}_3$$

N

$$= 0$$

(Vd)

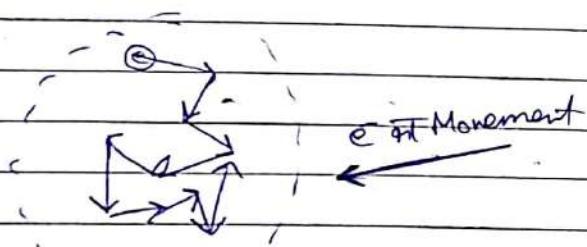


due to thermal energy

$$\frac{3}{2} kT = \frac{1}{2} m v^2$$

at room temp.

$$V = 10^6 \text{ m/sec}$$

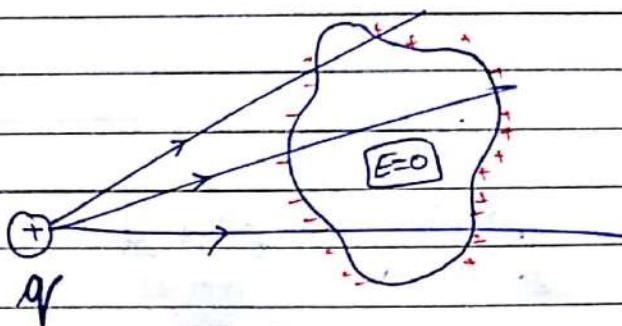

23.12

16/EO

18/

20/

16/

10/


22/

18/

$$J = n \cdot 10^6 \times 1.6 \times 10^{-19}$$

$$J = 10^6 \times 1.6 \times 10^{-19} \times n \times \frac{5 \times 10^{19-6}}{10^6 \times 1.6} = \frac{10 \times 5}{16} J$$

3.12

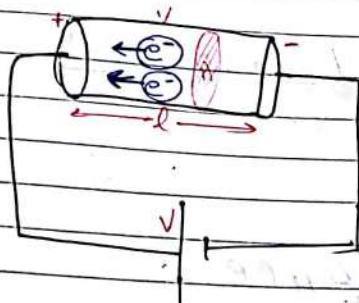

$$F = \frac{e}{l} \cdot V$$

Electron field

potentia off maintained.

$$(V_d = 10^{-3} \text{ m/sec})$$

(V) drift velo  $\rightarrow$  avg velo of  $e^-$

$$I = q A V_d n e$$


current flowing in conductor

no of  $e^-$  per unit volume

charged  $1e^-$

Q - find approx dist travelled by  $e^-$  in an electric field in which its distance displacement is 1m along the wire

$$V = 10^6 \text{ m/sec}$$

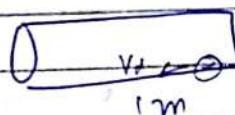

$$t = \frac{l}{V_d}$$


$$t = \frac{1}{10^3} = 10^3 \text{ sec.}$$

$$\text{dist} = V t$$

$$10^6 \times 10^3 = 10^9 \text{ m sec}$$

Relation b/w I & V in a conductor

Electron current  
Potential diff.  $V$

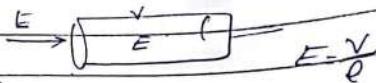

$$E = \frac{V}{L}$$

as we know

$$I = AV_dne \quad \textcircled{1}$$

area  
of cross  
section

expression for  $V_d$

$$\vec{F}_e = -e\vec{E}$$

$$\vec{a} = \frac{d\vec{v}}{dt} = -\frac{e\vec{E}}{m}$$

$$\int_v^v d\vec{v} = \int_0^t -\frac{e\vec{E}}{m} dt$$

$$\vec{v} - \vec{u} = -\frac{e\vec{E}}{m} \cdot t \quad \text{time interval b/w two successive collisions}$$

$$\vec{v} = \vec{u} - \frac{e\vec{E}}{m} \cdot t \quad \textcircled{2}$$

$$\vec{v} = \vec{u} - \vec{at}$$

$\vec{a}$   
due to random motion

note - drift velo is oppo of EF icon

Date: / /  
Page No.

V<sub>avg</sub> = drift velo

mean averaging

$$\langle \vec{V} \rangle = \langle \vec{U} \rangle - \frac{eE}{m} \langle t \rangle$$

$$V_d = 0 - \frac{eE}{m} \tau$$

$\tau$  → relaxation time

$$V_d = \frac{eE}{m} \tau$$

②

magnitude of drift velocity.

from ① & ②

$$I = A \left( \frac{eE}{m} \tau \right) n e \quad \left\{ E = \frac{V}{L} \right\}$$

$$I = A \frac{e^2 n \tau}{m} V$$

$$V = \left( \frac{m}{A e n \tau} \right)^{\frac{1}{2}}$$

$$V \propto I \quad \text{Ohm's law}$$

$$V = I R$$

$$R = \frac{m}{c^2 n T} \cdot \frac{l}{A}$$

$$R = \frac{\rho l}{A}$$

length  
area of cross section

Resistance of wire

conductivity of material/  
specific resistance,

$$\rho = \frac{m}{c^2 n T}$$

R depends on :-

- 1) geometry of wire
- 2) material
- 3) Temp. ( $\text{temp} \uparrow T \downarrow$ )

i.e.  $l, A,$   
 $n, T.$

$T \leftarrow$  depends on temp.

~~Note~~  $I = \frac{A c^2 n T}{m l} \cdot V$

$$\frac{I}{A} = \frac{c^2 n T}{m} \cdot E$$

$$\frac{V}{l} = E$$

Current density

$$J = \frac{E}{\rho}$$


$$\text{or } J = \sigma E$$

$$E = \rho J$$

current density  $(\frac{E^2 n T}{m})$  conductivity  $= \frac{1}{\rho}$
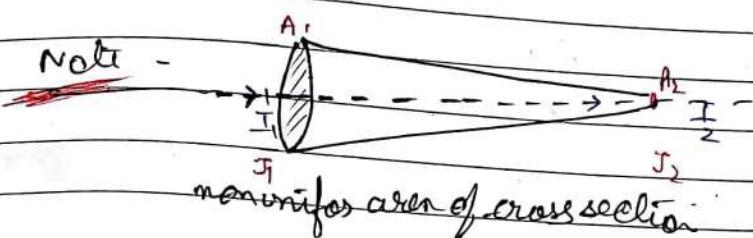
## Resistivity

In a DC circuit Resistivity is shown by —————



$I_1 = I_2 = I$  (Some)  $\rightarrow$  rate of flow of charge is same throughout the wire.


A Vane  $\xrightarrow[\text{const}]{}$  also  $\rightarrow$  some,

$\Delta \uparrow$  drift Velo. ✓

$$A_1 V_{d1} = A_2 V_{d2}$$

$$J_1 < J_2 \text{ as } (f = \frac{I}{A})$$

Q-

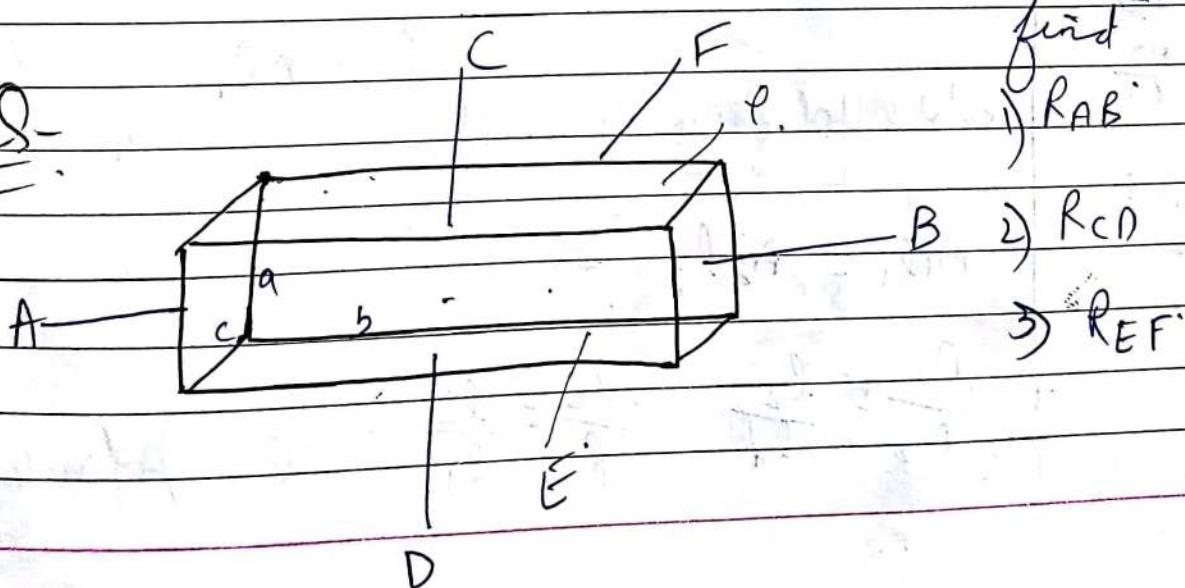

$$1) R_{AB} = \frac{\rho l}{A} = \frac{\rho b}{ac}$$

$$2) R_{CD} = \frac{\rho l}{A} = \frac{\rho a}{bc}$$

$$3) R_{EF} = \frac{\rho l}{A} = \frac{\rho c}{ab}$$

Q - A wire of resistance ( $R$ ) is stretched to double its length.  
Calculate its new resistance

$$V = I(R)$$

(QX)

$$R = \frac{\rho l}{A}$$

$$\frac{R_2}{R_1} = \frac{\rho_2 l_2}{\rho_1 l_1} \frac{A_1}{A_2}$$

(1)

assumption:

$$\frac{R_1}{R_2} = \frac{\rho_1 l_1}{\rho_2 l_2} \frac{A_2}{A_1}$$

as volume is same.

$$A_1 l_1 = A_2 l_2$$

$$\frac{l_1}{l_2} = \frac{A_2}{A_1}$$

$$\frac{R_1}{R_2} = \left( \frac{l_1}{l_2} \right)^2$$

$$A_1 l_1 = A_2 l_2$$

$$\frac{A_1}{A_2} = \frac{l_2}{l_1} \quad \frac{R_2}{R_1} = \frac{l_2}{l_1} \rightarrow (2) \text{ put in } (1)$$

$$4R_1 = R_2$$

$$\frac{R_2}{R_1} = \left( \frac{l_2}{l_1} \right)^2$$

$$\frac{R_2}{R_1} = \left( \frac{\alpha l_1}{l_1} \right)^2 \Rightarrow R_2 = 4R_1$$

Q3 - Wire is stretched to change its length by  $0.1\%$ . Calculate % change in resistance.

$$\frac{R_2}{R_1} = \left( \frac{l_1 + 0.1}{l_1} \right)^2 = \frac{1+0.1}{1} = 1.0(1+0.1)^2$$

$$\begin{aligned} & \frac{(0.1)}{10} \times 1 \quad (0.01) \\ & \frac{0.1}{10} \times 1 \quad 0.001 \\ & l_1 + (0.1)^2 \\ & \frac{1+1}{10} \frac{1}{10} \frac{1}{100} \end{aligned}$$

% change in resistance

$$\left( \frac{R_2 - R_1}{R_1} \right) \times 100$$

$$\begin{aligned} & \frac{(1.1)}{1.0} \\ & 1.1 \\ & 0.1 \end{aligned}$$

$$l_2 = l_1 + l_1 \times \frac{x}{100}$$

$$\frac{l_2}{l_1} = \left( 1 + \frac{x}{100} \right) \quad \text{--- (1)}$$

$$A_1 l_1 = A_2 l_2$$

$$\frac{R_2}{R_1} = \left( \frac{l_2}{l_1} \right)^2$$

$$R_2 = (1+x)^2$$

$$\left[ \left( 1 + \frac{x}{100} \right)^2 - 1 \right] \times 100$$

for ex - if length is increased by  $100\%$  then R increases by  $300\%$

& if  $x \rightarrow$  very small change

expanding binomially

$$\left( 1 + \frac{2x}{100} - 1 \right) \times 100$$

$$= 2x \quad \% \quad 0.2\%$$

Note -

$$R = \frac{\varphi l}{A}$$

$$\frac{\Delta R}{R} = \frac{\Delta \varphi}{\varphi} + \frac{\Delta l}{l} - \frac{\Delta A}{A}$$

(1)

$$V = A \cdot l = \text{const}$$

$$\frac{\Delta V}{V} = \frac{\Delta A}{A} + \frac{\Delta l}{l} = 0$$

$$\frac{\Delta l}{R} = 2 \frac{\Delta l}{l}$$

$$\left( \frac{\Delta R}{R} \times 100 \right) = 2 \left( \frac{\Delta l}{l} \times 100 \right)$$

$$= 2 \times 0.1$$

$$= 0.2\%$$

## Effect of temp

$\alpha$  — temp coeff of resistivity

$$\alpha = \frac{1}{\rho} \frac{d\rho}{dT}$$

fractional change in resistivity  
for per unit change in  
temp

$\rightarrow \alpha = \text{const}$

$$\int_{\rho_1}^{\rho_2} \frac{d\rho}{\rho} = \alpha \cdot \int_{T_1}^{T_2} dT$$

$$\ln \frac{\rho_2}{\rho_1} = \alpha (T_2 - T_1)$$

$$\boxed{\rho_2 = \rho_1 e^{\alpha (T_2 - T_1)}}$$

$\alpha$  exponentially increasing

$$R = \frac{\rho l}{A}$$

$\frac{l}{A}$  neglecting as its very small height

$$R_2 = R_1 e^{\alpha(T_2 - T_1)}$$

$$\text{if } \alpha(T_2 - T_1) \ll 1$$

$$R_2 = R_1 [1 + \alpha(T_2 - T_1)]$$


$$Se^{-\frac{x}{1+x+\frac{x}{Q_1}}}$$

neglect

$$R_2 = R_1 [1 + \alpha(T_2 - T_1)]$$

### Current in a resistance


high  $\rightarrow$  lower

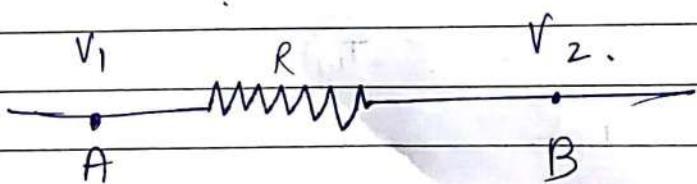

Current in resistance always flows from higher potential to lower potential.

①  $V_1 > V_2$


$$I = \frac{V_1 - V_2}{R}$$

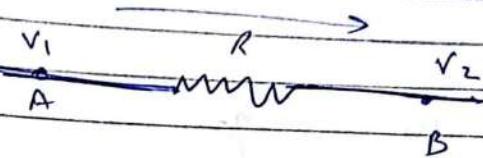

dir  $A \rightarrow B$

②  $V_2 > V_1$


$$I = \frac{V_2 - V_1}{R}$$

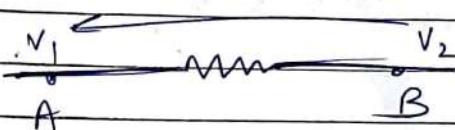

dir  $B \rightarrow A$
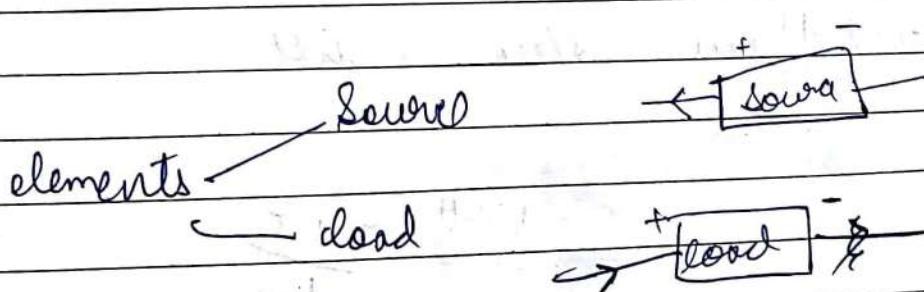
## Power in Electric Circuit

energy liberated in one second in any electric device is called its power.



full generation

PPRIT

$$I = \frac{dq}{dt} \quad (1)$$

$$dw = v \cdot dq$$

now will

$$\frac{dw}{dt} = v \frac{dq}{dt}$$

$$= VI$$

$$\text{rate of dissick} = VI$$

(P) Power =  $VI$

*Voltage* *Current*  
*Potential diff*

if power is constant

$$E = P \cdot t$$


energy libaral in time  $t$

→ power variable (i.e. function of time)

$$E = \int_0^t P dt$$

$$\text{unit of power} = J/\text{sec} \text{ or watt}$$

Power consumed in a resistor

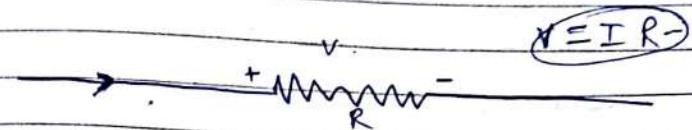


$$\boxed{P = VI} \\ = I^2 R$$

$$\boxed{P = I^2 R}$$

$$\text{or } \boxed{P = \frac{V^2}{R}}$$

Note


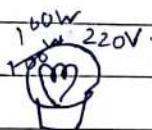


If connected to 220 volt then it will consume 100 W. / sec. / 100W power


Resistance of bulb .

$$R = \frac{V^2}{P} = \frac{(220V)^2}{100W} = 484 \Omega$$
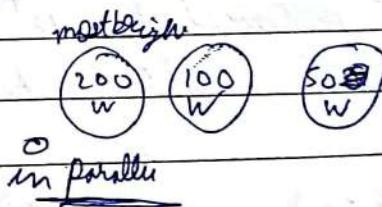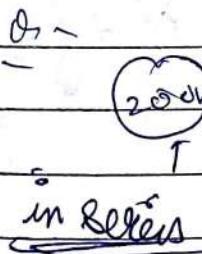
$$R = \frac{220 \times 220}{100} = 484 \Omega$$



5. Calculate power consumed by bulb

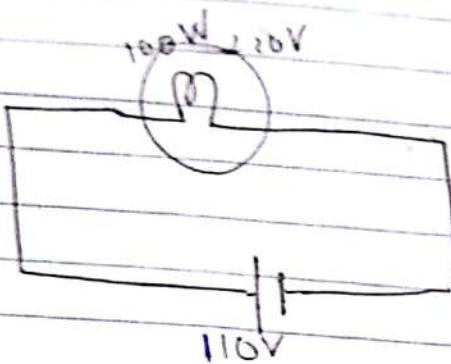

V<sub>Bulb</sub>  
from radio

$$R_B = \frac{(20)^2}{100} = 4 \Omega$$

$$\text{Power}_{\text{Bulb}} = \frac{V^2}{R_B} = \frac{(20)^2}{484}$$

~~50~~  
~~484~~

$$P_B = 25 \text{ W}$$


## Battery / Cell

It is a device which maintains a const potential diff across its terminals

battery is prepared by putting two rods of diff metal in a chemical solution,

chemical energy  $\rightarrow$  electric energy

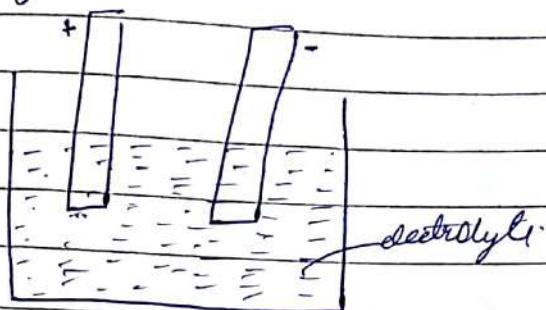battery force :  $F_b$  non electrostatic



electric field  $\rightarrow$  due to charges on lead  
(anode & cathode)


$$f_e = (q E) =$$

↓  
electrostatic force

at steady state

$$F_b = f_e$$

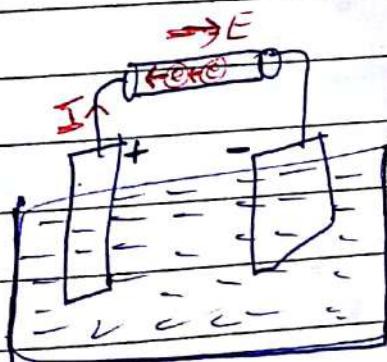battery force balances electrostatic force



charge in pure medium  
no battery jummed

Internal resistance of battery  
 depends on (i) New plan

- (i)  $r \propto d$  separation between plates
- (ii)  $r \propto c$  - conc of electrolyte

$$r \propto \frac{1}{S} \quad \rightarrow \text{area of plate}$$

$$r \propto \frac{1}{T} \quad T = \text{temp}$$


→ meaning of 10 amp/hr.  
 (battery is 10 amp hr at 10 shanti chahay)

if 10 amp current is withdrawn from the battery  
 then it will work for 1 hour


or 1 amp  $\rightarrow$  10 hrs.

$\frac{1}{2}$  amp  $\rightarrow$  20 hrs

Electromotive force.

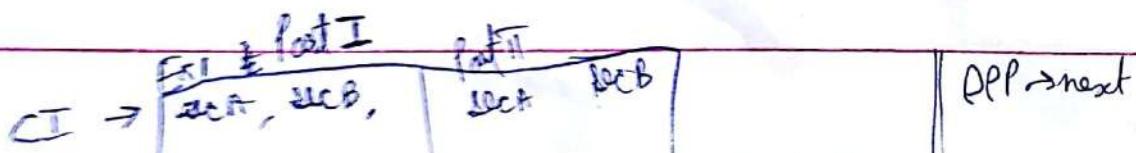

## Electromotive force (EMF) of battery

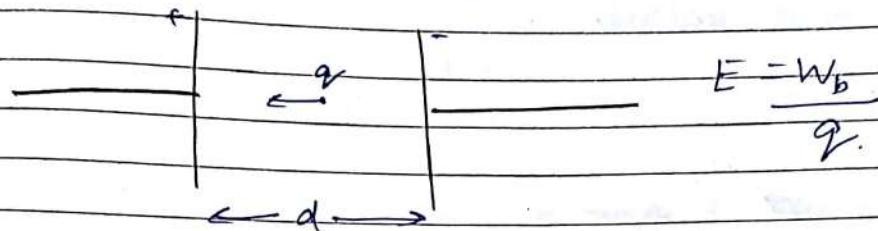

$$E = \frac{W_B}{q}$$

It is the work done by battery per unit charge

unit = Joule/Coulomb = Volt (V) like Potential diff. unit

\* when cell is not externally connected ( $F_B = F_E$ )

$$= q E$$

electric field.

$$W_B = F_B \cdot d$$

$$= (q E \cdot d)$$

$$W_B = q \cdot V$$

$V$  = potential diff

EMF


$$E = \frac{q \cdot V}{q} = V$$

work done  
per unit charge

$$E = V$$




Note

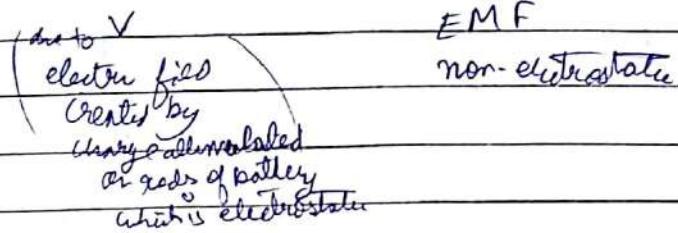$\text{EMF}$  & Potential diff are two different quantities.  
 $\text{EMF}$  is work done by battery force which  
 is non-electrostatic.



& potential diff is produced by electric fields due to charges accumulated on plates which is conservative.

Representation of battery

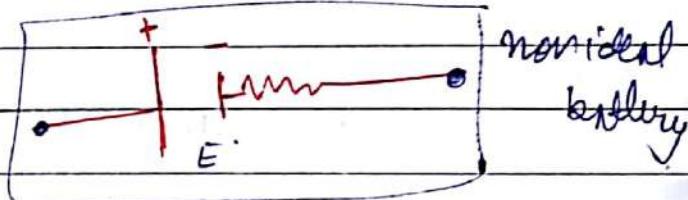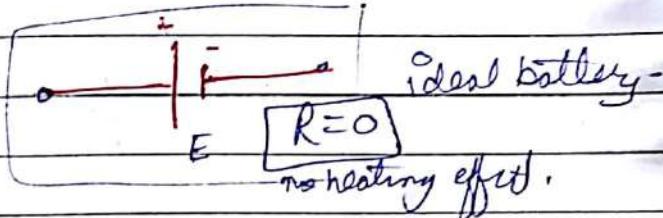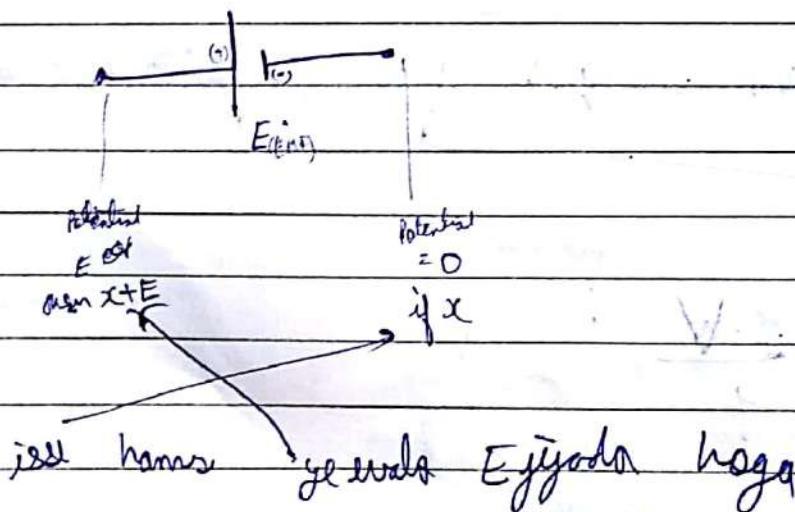Note

$$V_A - V_B = \text{terminal voltage of battery}$$

→ +ve side near to Source

25-

icon

Date: 1/1/14


Page No.

## Battery as a Source

$$V_A - IR = V_B$$

$$V_A - V_B = E - IR$$

$$\text{terminal voltage} = E - IR$$

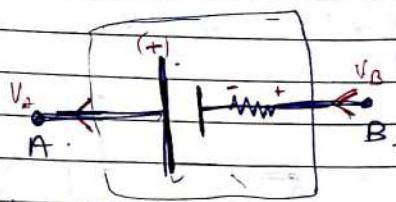

Emf & short

the rate at which the chemical energy is consumed  
in battery =  $EI$

current flowing

$$EI - I^2R$$

↓ internal

the rate at which heat is generated  
with

$$\text{no output power.} = EI - I^2R$$

so output power = Energy supp - heat used

$$(EI - I^2R) - EI = -I^2R$$

$$+ (EI - IR)$$

$$I(E - IR)$$

from ①

$$P =$$

$$\boxed{I(V_B - V_A)}$$

current × terminal voltage


$$V_{ads} = I$$

$$I = 0.8 \times V$$

$$3.2 = 5 \times 10^3 \times X$$

$$X = \frac{3.2}{5 \times 10^3}$$

Battery acting as load

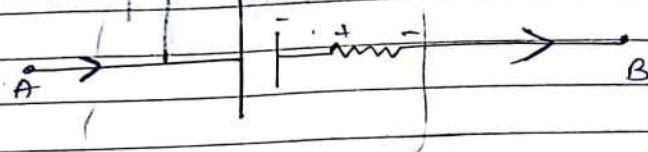

$$V_A - E - IR = V_B$$

$$V_A - V_B = E + IR$$

EMF & load in battery

the rate at which chemical energy is stored is  $EI$

(from longer to medium miles)  $I^2R$  for heat generation

Power dissipated  $= I^2R$

Input power  $= EI + I^2R$ ,  
(power given to battery)


$$P = I(E + IR)$$

$$P = I(V_A - V_B)$$

Ans.

Note

open  
circuit

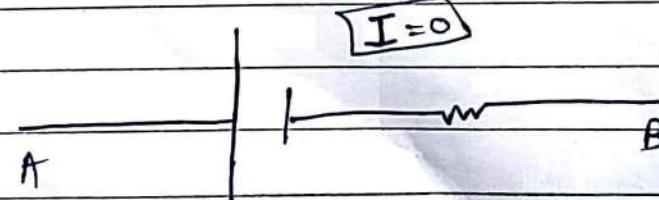

thus

$$(V_A - V_B) = E$$


$$P_{\text{av}} = \frac{V}{R} I$$

from  
eq

**iron**

Date: / /  
Page No.

short circuit

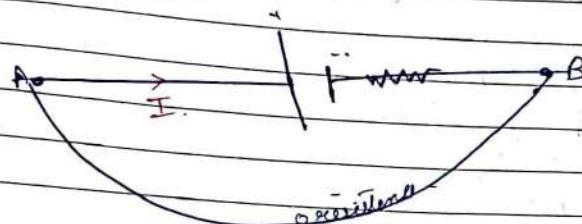

connected by zero resistance.

$$V_A = V_B = 0 \quad \leftarrow I = \frac{E}{R} = 0$$


$$V_A = V_B$$

$$\text{terminal voltage} = V_A - V_B = (E - IR) = 0$$

$$E = IR$$

$$\boxed{\text{current } I = \frac{E}{R}}$$

Max power transfer theorem

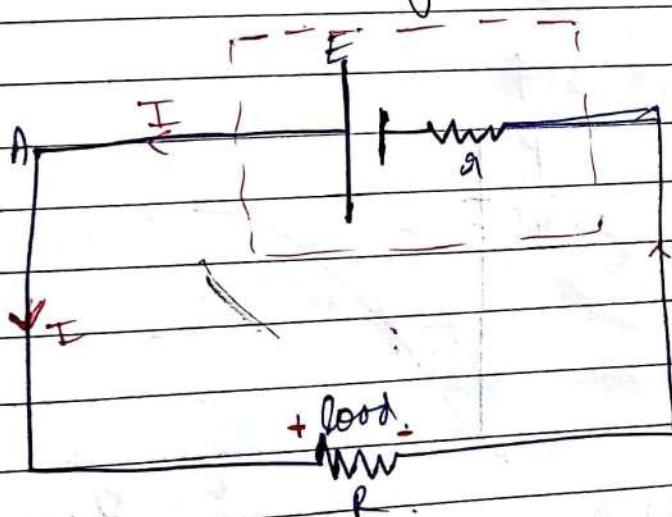

$$\text{terminal voltage of cell} \quad V_A - V_B = E - IR \quad \text{--- (1)}$$

$$I = \frac{V_A - V_B}{R} \quad \text{--- (2)}$$

from (1) & (2)

$$\boxed{I = \frac{E}{R + r}}$$

not EMF  
total resistance

Power delivered in load.

$$\begin{aligned} P &= I^2 R \\ &= \frac{E^2 R}{(R+r)^2} \end{aligned}$$

for max power in load  $R$


$$\frac{dP}{dR} = 0$$

$$\frac{d}{dR} \left[ \frac{R}{(R+r)^2} \right] = 0$$

diff

$$R = r$$

$$P_{\max} = \frac{E^2}{4r^2}$$

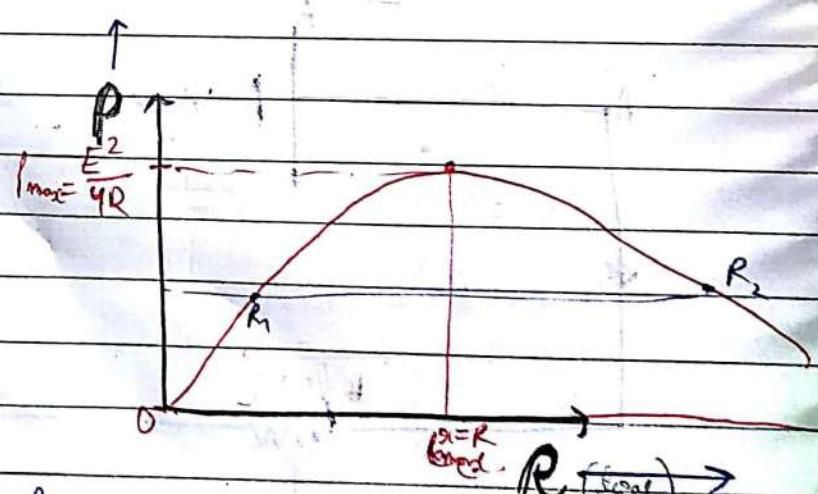

$$R = R_1 \quad R = R_2$$

Power same.

$$R(R+r)^2 - E^2 R = 0$$

expand:

$$R(R^2 + r^2 + 2Rr) - E^2 R = 0$$

$$R^2(2r - E^2) + Rr^2 = 0 \quad \left. \begin{array}{l} R_1 \\ R_2 \end{array} \right\}$$

quad eq whose roots are  $R_1$  &  $R_2$ .

~~$$R_1 R_2 = r^2$$~~

$$r = \sqrt{R_1 R_2}$$

### EFFECTIVE EFFICIENCY OF CELL

output power

= total energy spent by battery

$$\frac{I^2 R}{I^2 R + I^2 r} \times 100\%$$

$$\left( \frac{R}{R+r} \right) \times 100$$

at max power 56% efficiency


$$\frac{60}{60+r} \times 100$$

$V_1 > V_2$

$$I = \frac{V_1 - V_2}{R}$$

Date: \_\_\_\_\_  
Page No. \_\_\_\_\_

### Circuit problems

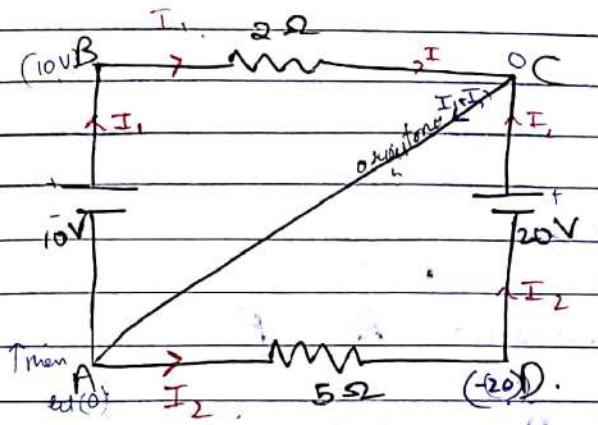

$$\left( \begin{array}{c} \text{+} \\ \text{-} \end{array} \right)$$

$$\left( \begin{array}{c} \text{+} \\ \text{-} \end{array} \right) \text{ at } 20$$

Find current in each branch of circuit.


$$I_1 = \frac{10-0}{2} = 5 \text{ A} \checkmark$$

$$I_2 = \frac{0-(-20)}{5} = 4 \text{ A} \checkmark$$


$$\text{Thus current in CA} = I_1 + I_2 = 5 + 4 = 9 \text{ A}$$

This we solved by zero potential method

Q

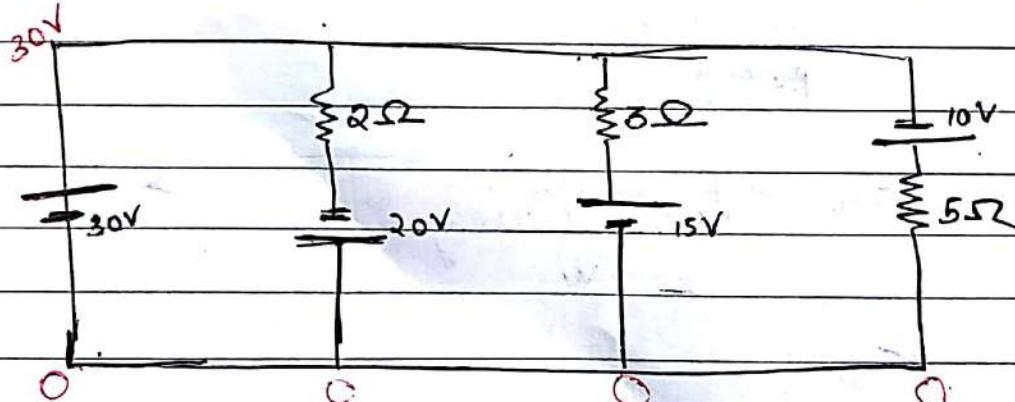


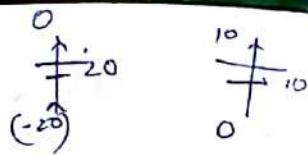Current flowing in each branch of circuit



icon

Date: 1/1  
Page No.

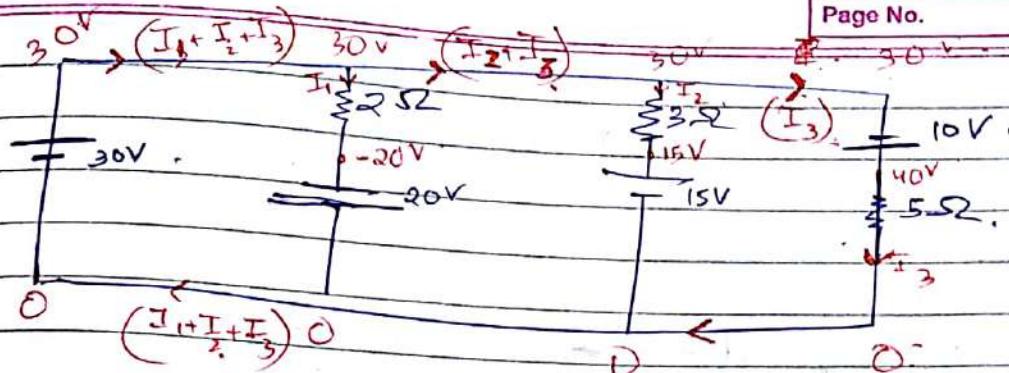

$$I_1 = \frac{30 - (-20)}{2} = 25 \text{ A}$$


$$I_2 = \frac{30 - 15}{3} = 5 \text{ A}$$

$$I_3 = \frac{40 - 0}{5} = 8 \text{ A}$$

Kirchoff's law for current distribution

⇒ Kirchoff current law (KCL) / Junction law

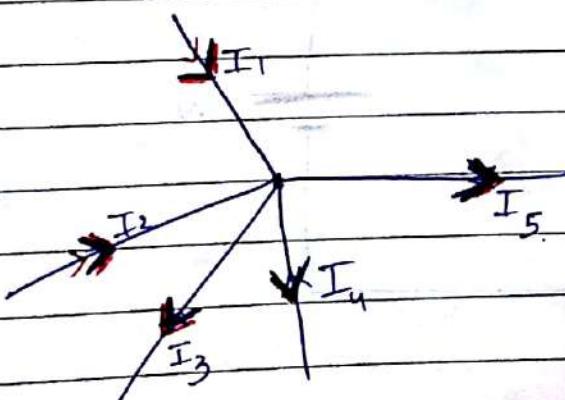It is based on the conservation of charge.



the algebraic sum of all current meeting at a point (junction)


In any electric circuit  $\sum I$  is always zero.

if  $\sum I = 0$


$$\text{by KCL} \Rightarrow I_1 + I_2 + I_3 - I_4 - I_5 = 0.$$

$$I_1 + I_2 = I_3 + I_4 + I_5$$

(it is by)

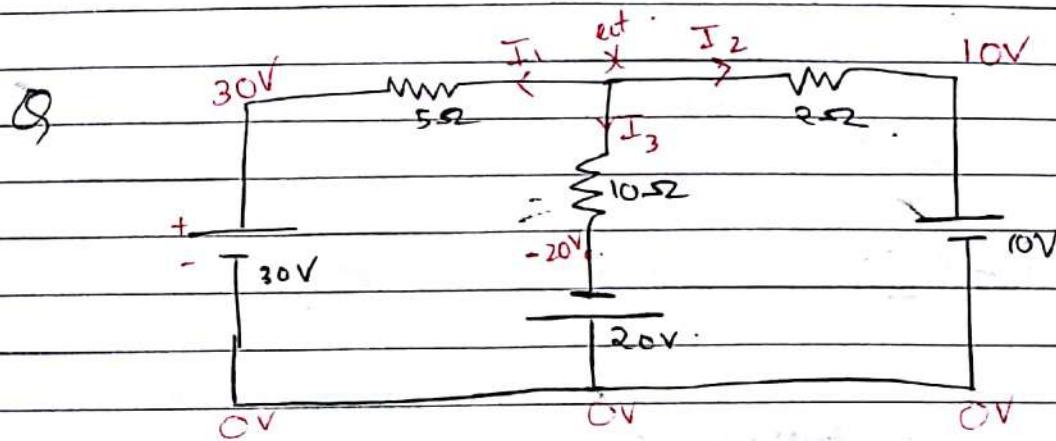

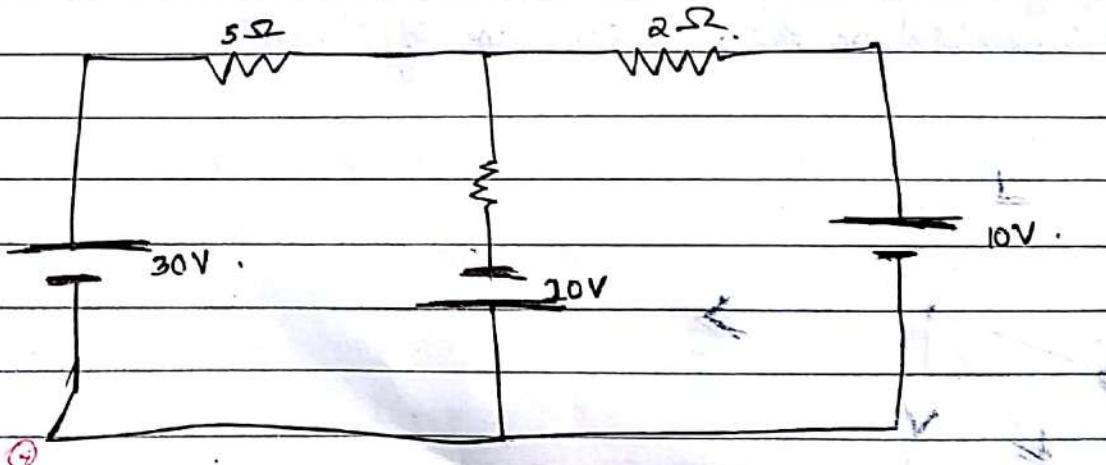find current flowing in each branch of circuit



using KCL

$$I_1 + I_2 + I_3 = 0.$$

$$\frac{(x-30)}{5} + \frac{x-10}{2} + \frac{x-(-20)}{10} = 0.$$

$$\frac{2x-60+5x-50+x+20}{10} = \frac{8x-90}{10} = 0.$$

$$x = \frac{90}{8} = \frac{45}{4} \text{ V}$$

now


$$I_1 = \frac{\left(\frac{45}{4} - 30\right)}{5} = -\frac{45 - 30 \times 4}{4} = -\frac{75}{20} = -\frac{15}{4} \text{ A}$$

thus < wali sign nahi  $I_1 \rightarrow$  ja rhi he.


$$I_2 = \frac{\frac{45}{4} - 10}{2} = \frac{5}{8} \text{ A.} \quad \text{thus } >$$

$$I_3 = \frac{\frac{45}{4} + 20}{10} = \frac{125}{40} \text{ A.} \quad \checkmark \text{ ja rhi he}$$

Q-

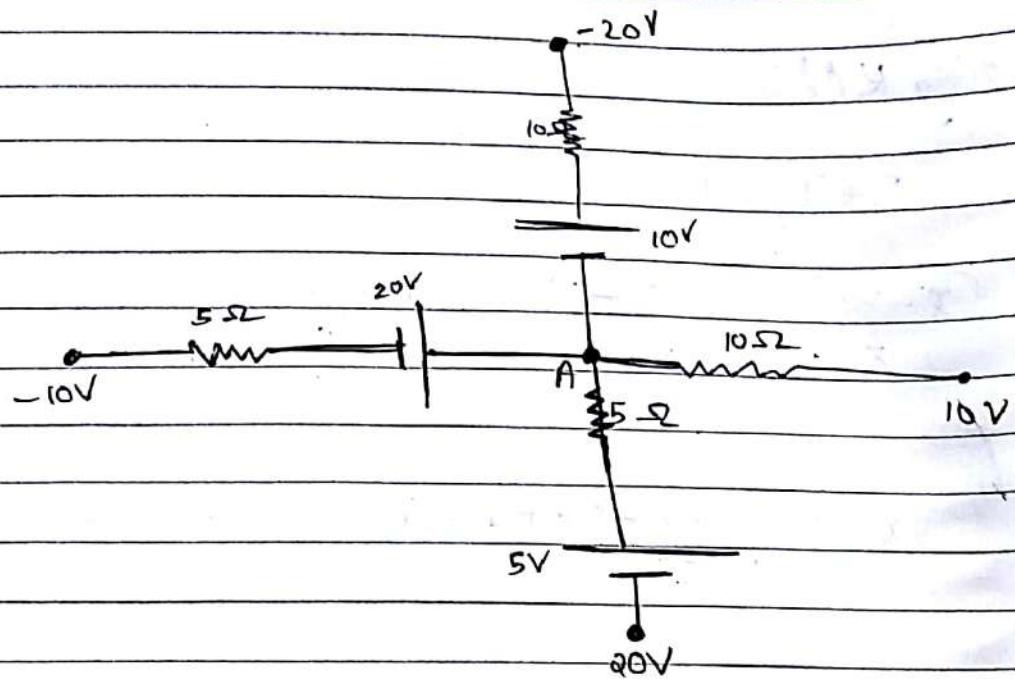

Calculate potential of point A

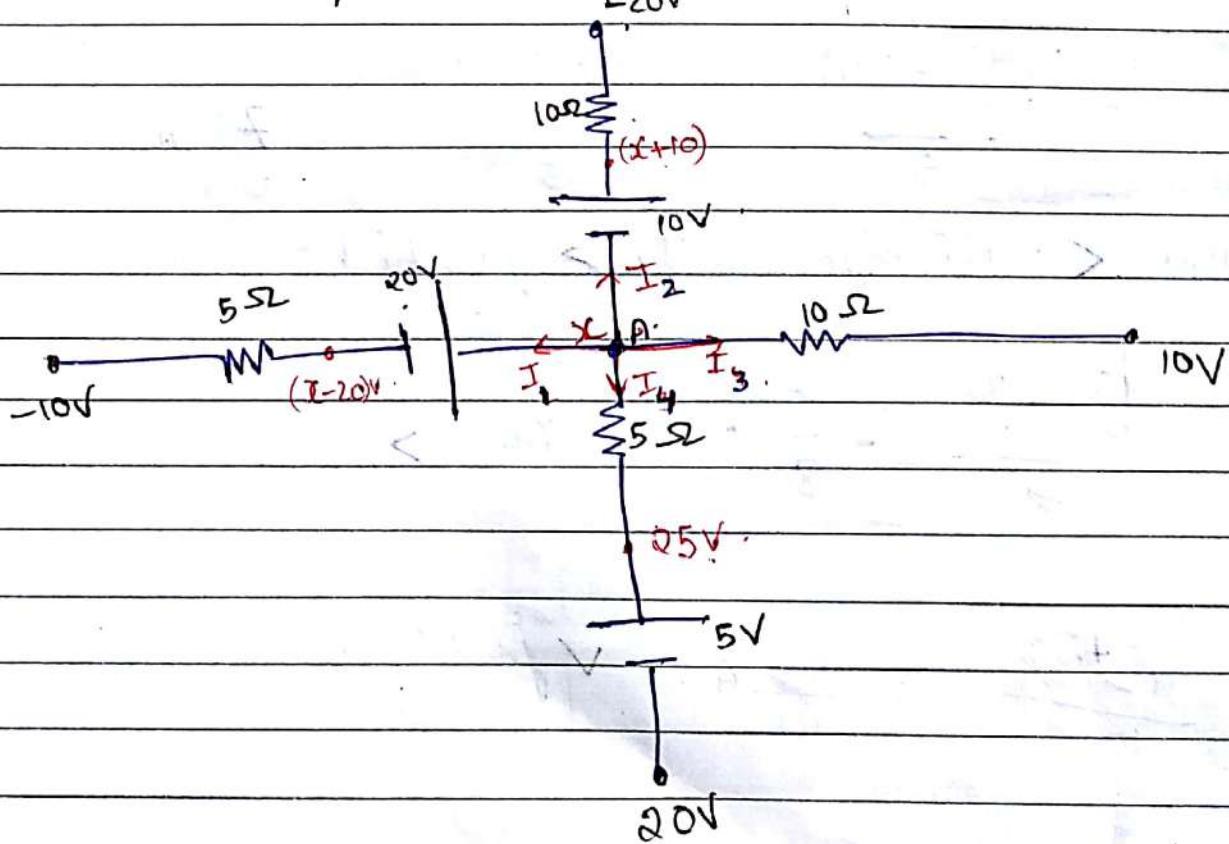

$$I_1 + I_2 + I_3 + I_4 = 0.$$

$$\text{KCL} = \frac{20}{x-20+10}$$

$$\text{KCR} = \frac{x-20+10}{5} + \frac{x+10-(-20)}{10} + \frac{x-10}{10} + \frac{x-25}{5} = 0$$

$$x = \frac{25}{3}$$

### Kirchoff Voltage law KVL

based on cons of energy


It is based on conservation of energy.

the algebraic sum of potential differences across each element in any closed path or loop in any circ circuit is ~~zero~~ always zero


∴

$$\sum \Delta V = 0$$


→ can be battery or junction

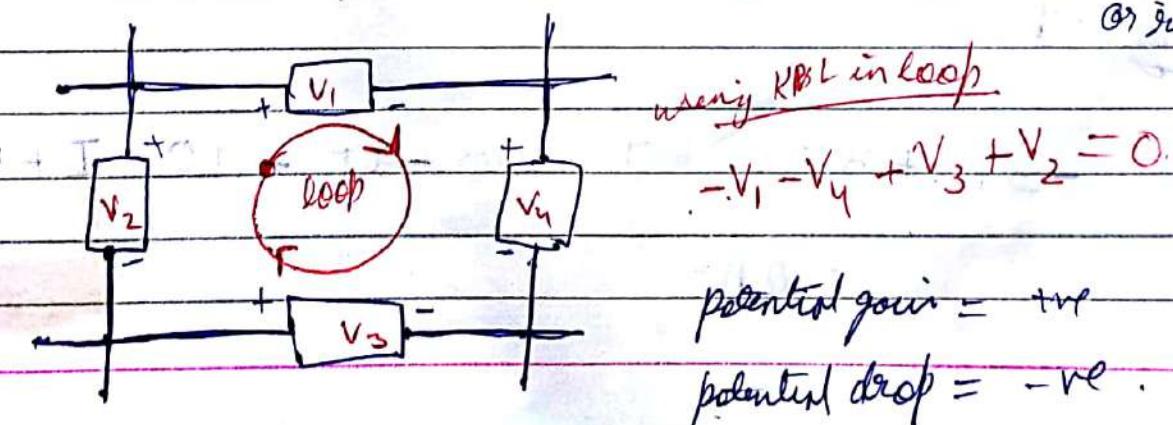

Q -

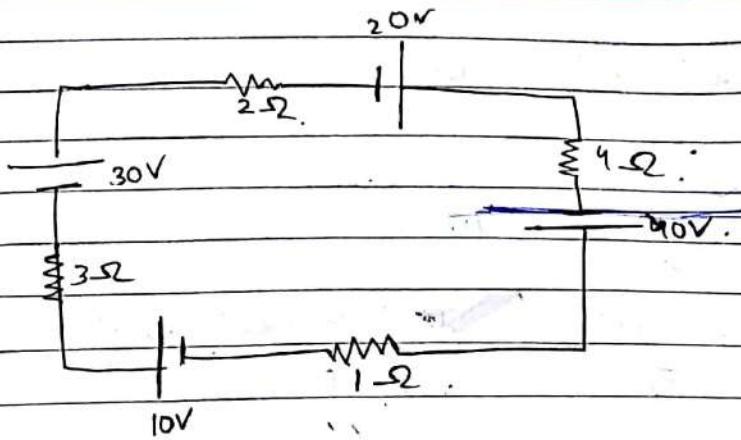

find current flowing in electric circuit

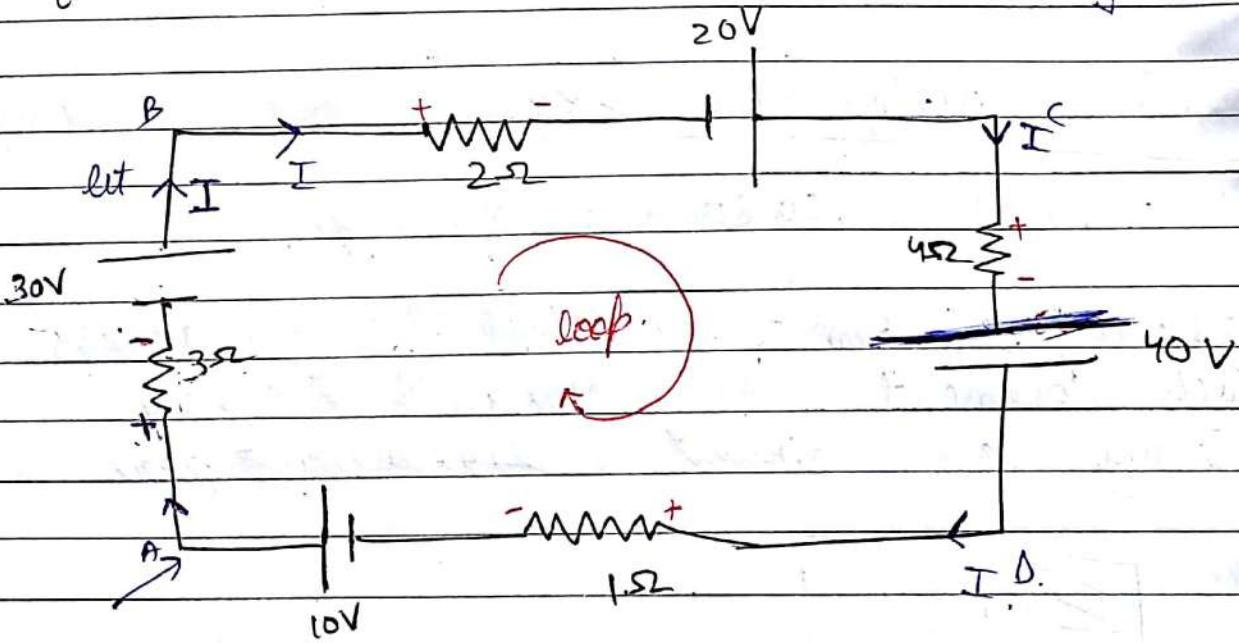

let current I flow thru circuit

$$N = IR$$

by KVK

$$-3I + 30 - 2I + 20 - 4I - 40 - I + 10 = 0$$

$$I = 2A$$



find  $V_B - V_D$  or also find diff of potential of pt B & potentiog pt D

$$V_B = -2I + 20 - 4I - 40 = V_D$$

put value of  $I = 2A$ .

$$V_B = 4 + 20 - 8 - 40 = V_D$$

$$V_B - V_D = 3\Omega$$

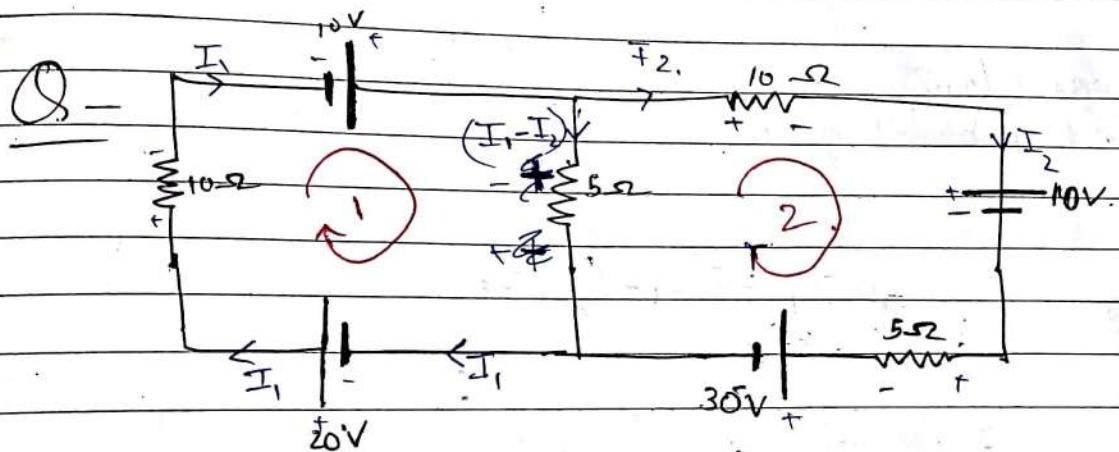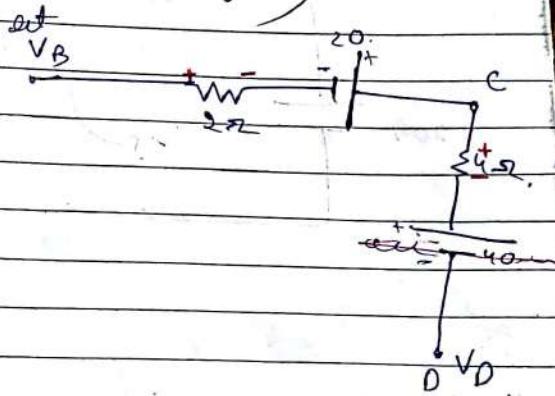

find current in each branch of Circuit

let current flow is  $I$ ,

by KVL

in loop ①

$$-10I + 10 - 5(I_1 - I_2) + 20 = 0$$

$$3I_1 + I_2 = 6 \quad \text{①}$$


in loop ②

$$-10I_2 - 10 - 5I_2 - 30 + 5(I_1 - I_2) = 0$$

$$I_1 - 4I_2 = 8 \quad \text{②}$$

by ① & ②  $I_1 = \frac{16}{11} A$   $I_2 = \frac{18}{11} A$

(Q)

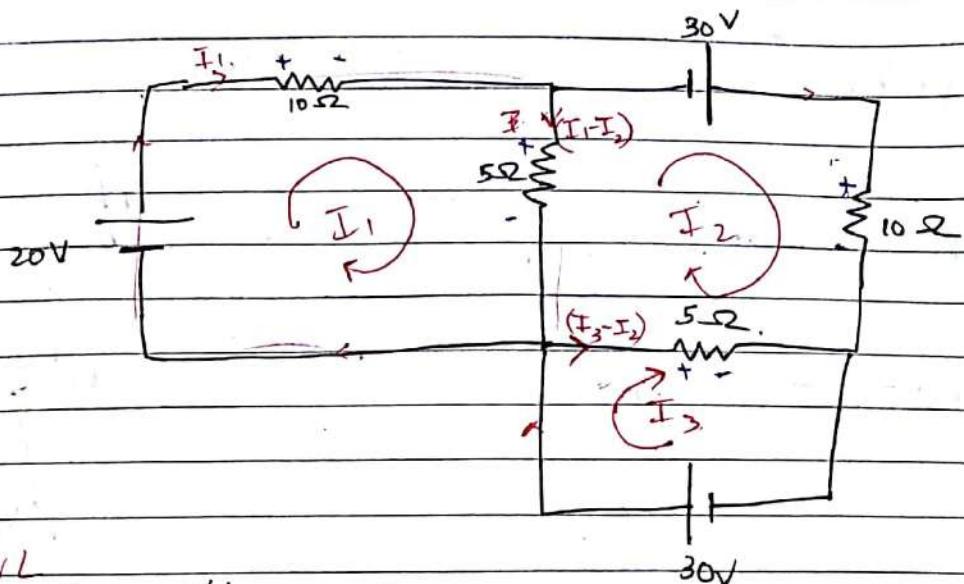

KVL

Q = Current flowing in each branch of circuit

using KVL loop 1.

$$+20 - 10I_1 - 5(I_1 - I_2) = 0 \quad \rightarrow (1)$$

loop 2

$$30 - 10I_2 + 5(I_3 - I_2) + 5(I_1 - I_2) = 0 \quad \rightarrow (2)$$

loop 3

$$-5(I_3 - I_2) + 30 = 0 \quad \rightarrow (3)$$

from (1) & (2) & (3)


~~$I_1 = 3$~~

~~$I_2 = 5$~~

~~$I_3 = 11$~~


100%

EX-1

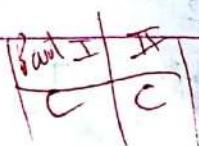

## Q - Combination of resistances

1) Series (end to end connect)

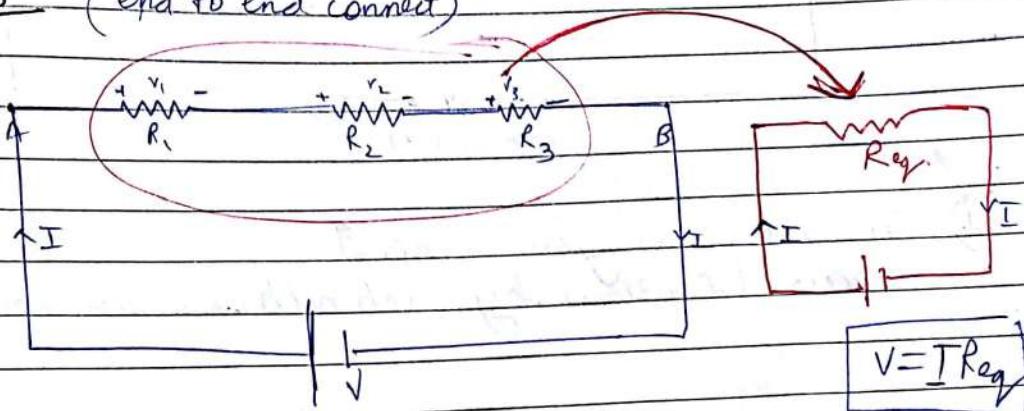

$$V = IR_{eq}$$

2) Using KVL

$$V - V_1 - V_2 - V_3 = 0$$

$$V = V_1 + V_2 + V_3$$

$$IR_{eq} = V_1 + V_2 + V_3$$

$$IR_{eq} = IR_1 + IR_2 + IR_3$$

$$R_{eq} = R_1 + R_2 + R_3$$

$$V_1 = IR_1 = \frac{VR}{R_{eq}} = \frac{VR_1}{R_1 + R_2 + R_3}$$

$$V_2 = IR_2 = \frac{VR_2}{R_1 + R_2 + R_3}$$

$$V_1 : V_2 : V_3 = R_1 : R_2 : R_3$$

10

$$P_1 = I^2 R_1$$


$$P_2 = I^2 R_2$$

$$P_3 = I^2 R_3$$

$$P_{\text{net}} = I^2 R_{eq}$$

$$P_1 : P_2 : P_3 = R_1 : R_2 : R_3$$

(Q)

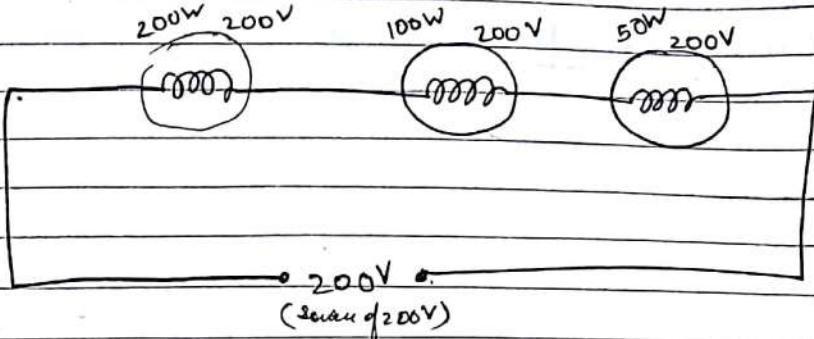

2) Parallel

1) Current flowing in circuit.

2) Power consumed by each bulb (which will burn more lights).

$$\frac{P = I^2 R}{I^2} = \frac{(200)^2}{200} + \frac{(200)^2}{100} + \frac{(200)^2}{50}$$

$$R = 200 \quad 400 \quad 800$$

$$R_{eq} = 1400$$

$$\frac{200}{100} = \frac{2}{1}, \frac{200}{50} = \frac{4}{1}$$

XCL

$$R_1 = \frac{(200)^2}{200} = 200, \quad R_2 = \frac{(200)^2}{100} = 400, \quad R_3 = \frac{(200)^2}{50} = 800$$

$$I = \frac{200}{R_1 + R_2 + R_3} = \frac{200}{1400} = \frac{1}{7}$$

$$V = 18 \text{ as } P = I^2 R$$

$$P_1 = I^2 R_1 = \left(\frac{1}{7}\right)^2 \times 200$$


$$P_2 = I^2 R_2 = \left(\frac{1}{7}\right)^2 \times 400$$

$$P_3 = I^2 R_3 = \left(\frac{1}{7}\right)^2 \times 800$$

most brightest

$$P_3 > P_2 > P_1$$

most power consumption

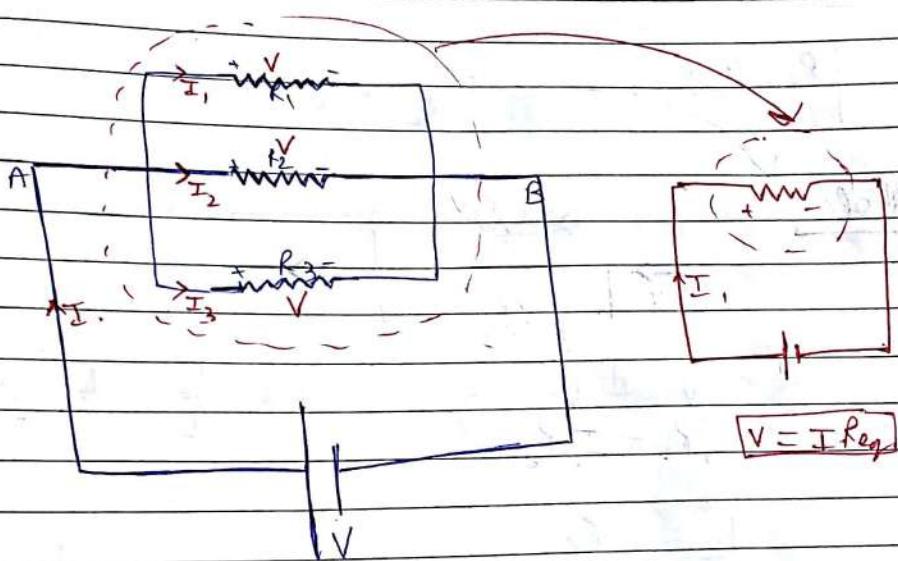2) Parallel Combination

KCL

$$I = I_1 + I_2 + I_3$$

$$\frac{V}{R_{eq}} = \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3}$$

$$I_1 = \frac{V}{R_1} = \frac{IR_{eq}}{R_1} = \frac{I}{\frac{R_1}{R_{eq}}} = \frac{I}{\frac{1}{G_1}} = \frac{IG_1}{G_1 + G_2 + G_3}$$

$G_1 = \frac{1}{R_1}$

conductance


$$I_2 = \frac{I}{\frac{R_2}{(R_1 + R_2 + R_3)}} = \frac{IG_2}{G_1 + G_2 + G_3}$$

$$I_3 = \frac{I}{\frac{R_3}{(R_1 + R_2 + R_3)}} = \frac{IG_3}{G_1 + G_2 + G_3}$$

$$I_1 : I_2 : I_3 = \frac{1}{R_1} : \frac{1}{R_2} : \frac{1}{R_3}$$

$$R_1 : R_2 : R_3 = \frac{1}{I_1} : \frac{1}{I_2} : \frac{1}{I_3}$$

Note -

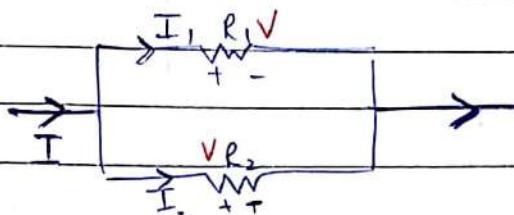

$$V = V$$

$$I_1 R_1 = I_2 R_2$$

$$I = I_1 + I_2$$

$$\frac{I_1}{I_2} = \frac{R_2}{R_1}$$

$$\frac{I_1}{I_1+I_2} = \frac{R_2}{R_1+R_2}$$

$$I_1 = \frac{IR_2}{R_1+R_2}$$

$$I_2 = \frac{IR_1}{R_1+R_2}$$

113  
116  
119



$$\frac{a}{b} = \frac{c}{d}$$

~~Electronics~~

icon



Date: / /  
Page No.

Q -

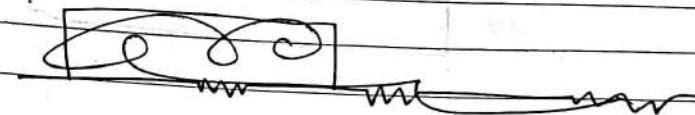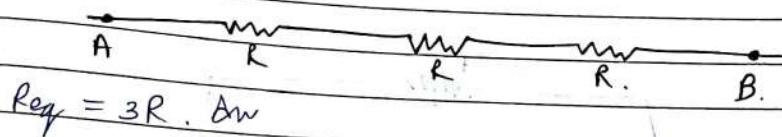

Q Calculate  $Req$  b/w A & B (zero resistance wire is used)


Simple help

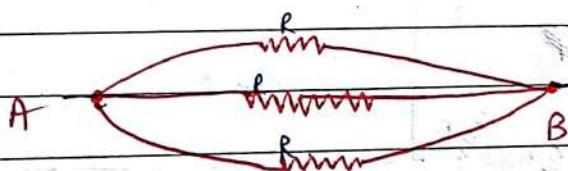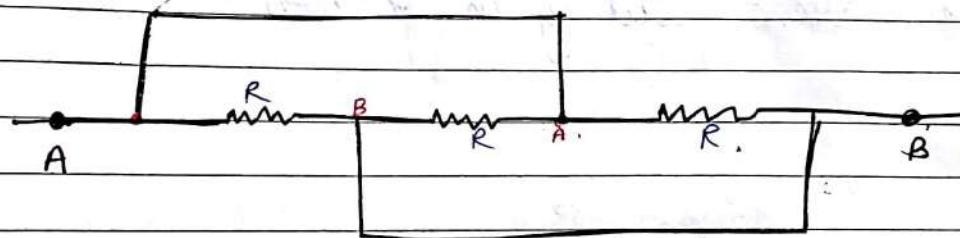

$$Req = R \times \frac{3}{3}$$


$$\frac{1}{R} = \frac{1}{R} + \frac{1}{R} + \frac{1}{R} = \frac{3}{R}$$

$$R = \frac{R}{3}$$

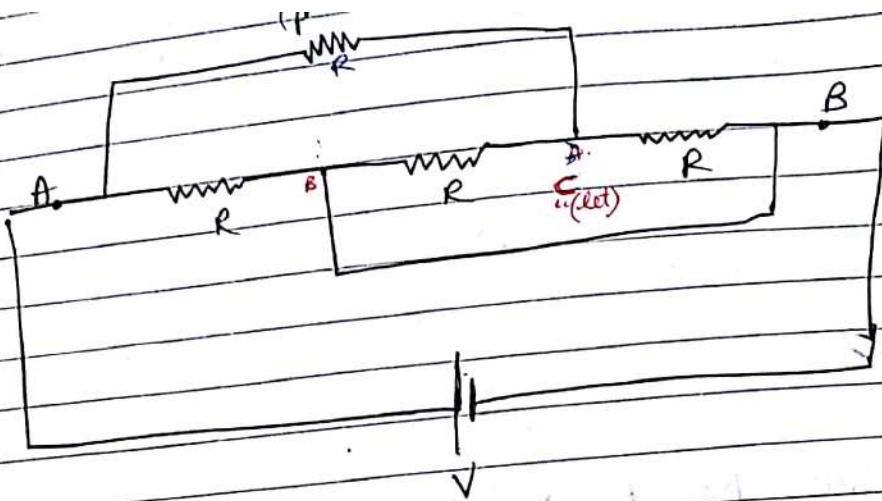

find current flowing in resistor P


~~dc across B.~~ A — w — B

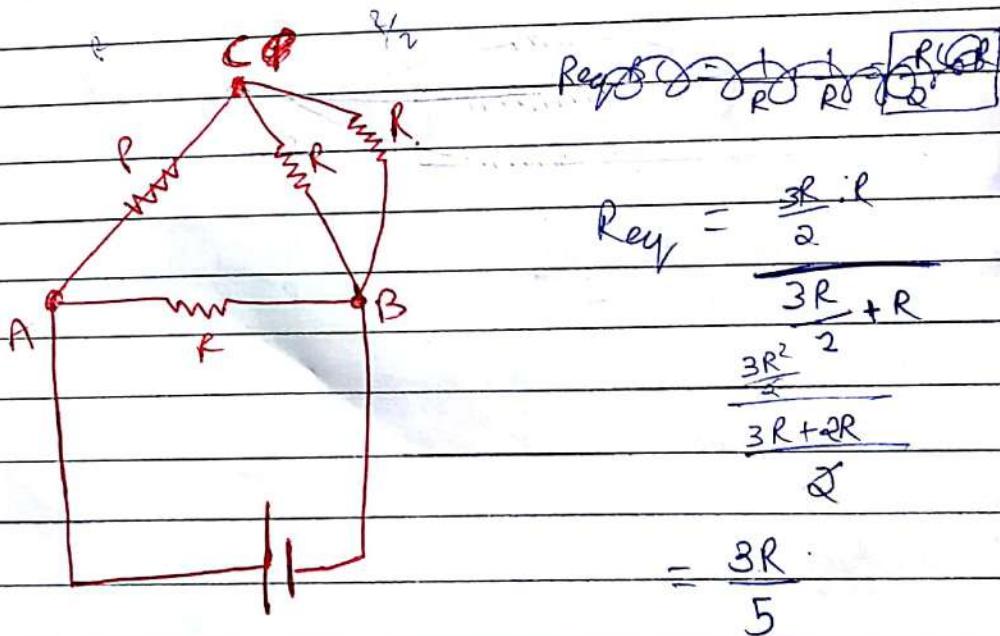

$$I = \frac{V}{R_{eq}} = \frac{5V}{3R}$$

2A  
5R

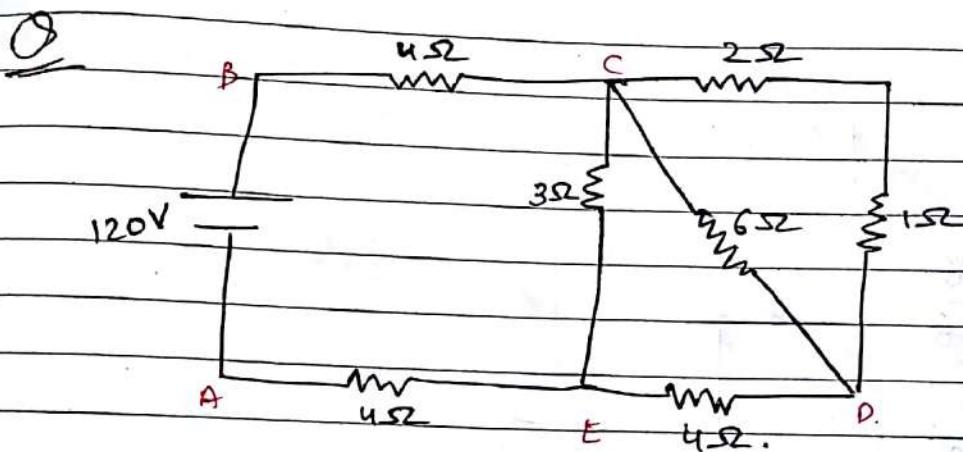ther  $I_t = \frac{IR}{R+3R} = \frac{2I}{3R}$  or  ~~$\frac{5V}{3R}$~~   $\frac{2V}{3R}$ .



find current flowing in 2 ohm resistance.


$$\frac{15}{\sqrt{60}} \cdot \frac{1}{20}$$

$$CD \quad \frac{3 \times 6}{3+6} = 2 \Omega$$

$$\frac{1}{2} + \frac{1}{2} \quad \frac{1+2}{2} \quad \frac{3}{2}$$

at end
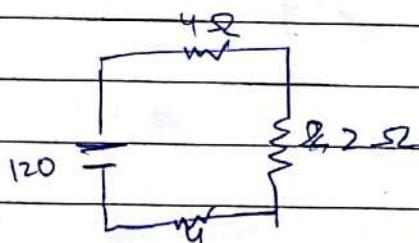
$$\frac{2}{3} + \frac{6}{3} \quad \frac{1}{3} + \frac{18}{3} \quad \frac{20}{3}$$



$$\frac{1}{3+4} + \frac{3}{20}$$

$$\frac{20+18+9}{60}$$

$$U \frac{6.0}{6.0} \frac{6.0}{6.0}$$

$$\frac{U}{60}$$

$$120A = I \cdot 10$$


$$I = 12A$$

$$8 + \frac{6.0}{6.0} \quad \frac{3}{9+32} \quad \frac{8}{32}$$

$$\frac{35.2+6.0}{44}$$

$$\frac{10.3}{44} \quad \frac{44.2}{44}$$

$$\frac{11 \times 120}{103} = I$$

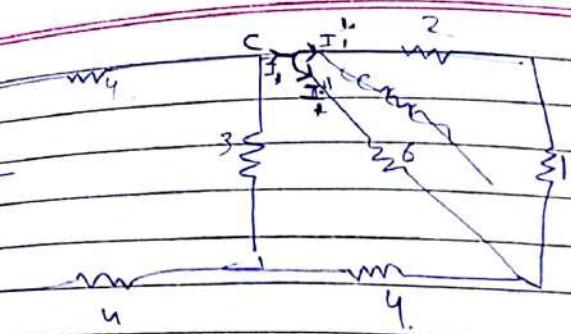

$$I_1 = \frac{12 \times 3}{3+6}$$


$$I_1 = 4A$$

$$I_1' = \frac{4 \times 6}{3+6}$$

$$I_1' = \frac{8}{3} A$$

# Cathet Stone bridge

4 terminal device

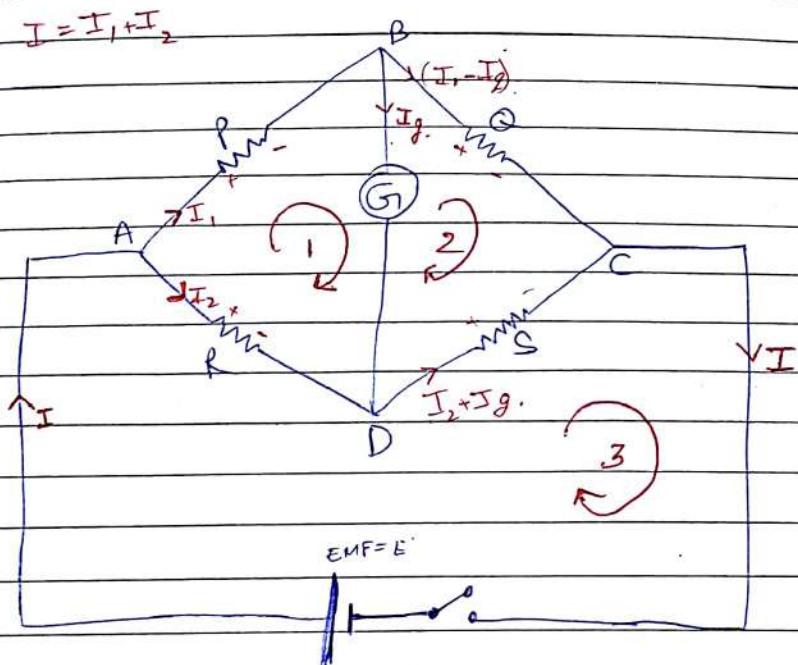

if  $I_g = 0$

wheatstone bridge is balanced.

$$V_B = V_D$$

$$V_A - V_B = V_A - V_D$$

$$V_B - V_C = V_B - V_C$$

$$I_1 P = I_2 R$$

$$I_1 Q = I_2 S$$

— ①


— ②

Q/B -


divide

$$\frac{P}{Q} = \frac{R}{S}$$

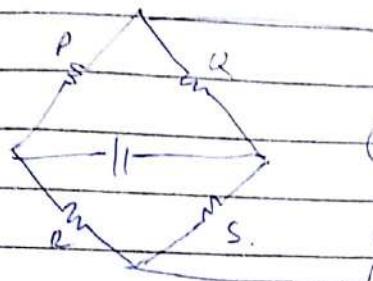if position of galvanometer & battery are interchanged  
then null point remains  
(cond of zero deflection)




unaffected

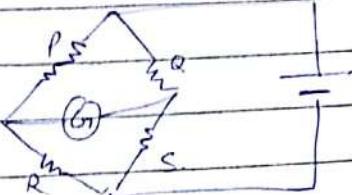

$$\frac{P}{Q} = \frac{R}{S}$$

unaffected

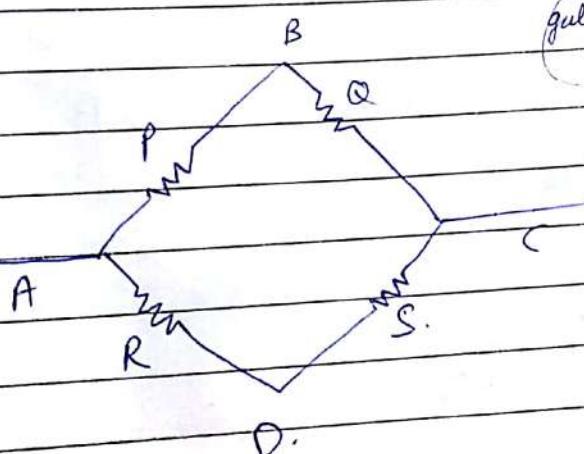for Calculation of Equivalent resistance across  
A & C




gali is galvano ya niki bhū hotoye use  
rai to farak fastamhi  
they are in series

$$\frac{1}{R_{AC}} = \frac{1}{P+Q} + \frac{1}{R+S}$$


as B, D Potential same  
resistance will add

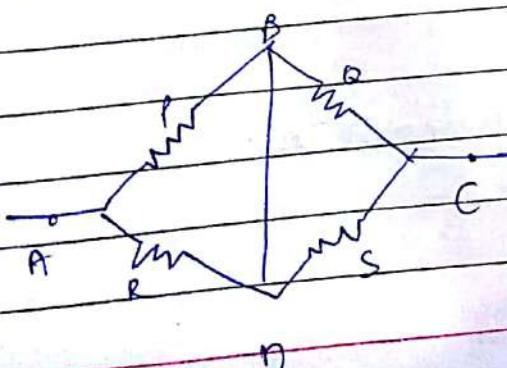P, R parallel, Q, S parallel.  
add then they are in series



$$R_{AC} = \frac{PR}{P+R} + \frac{QS}{Q+S}$$

NOTE

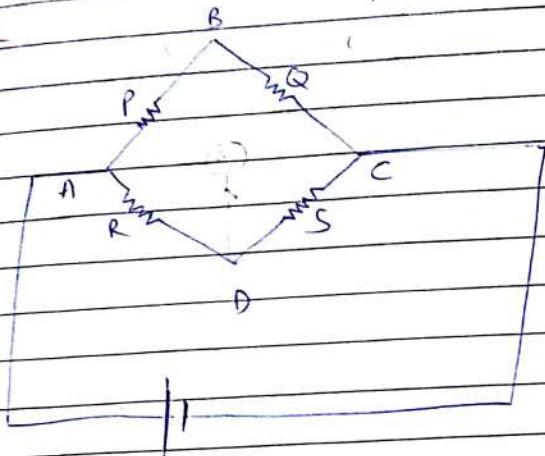

if  $V_B < V_D$   
2 galvanometer added them D to B current flow hogni

if  $V_D > V_B$   
current will flow from D to B

$$V_A - V_D < V_A - V_B$$

Var-

$$\frac{V}{R+S} \cdot R < \frac{V}{P+Q} \cdot P$$

(current)

current = I

$$R(P+Q) < P(R+S)$$

$$\text{if } PS > RQ$$


then current will flow from D to B - (1)

$$\text{then } P > V_B < V_D - (2)$$



read

3

(Q)

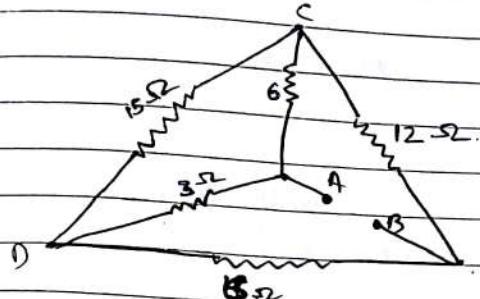

Equivalent resistances across A & B

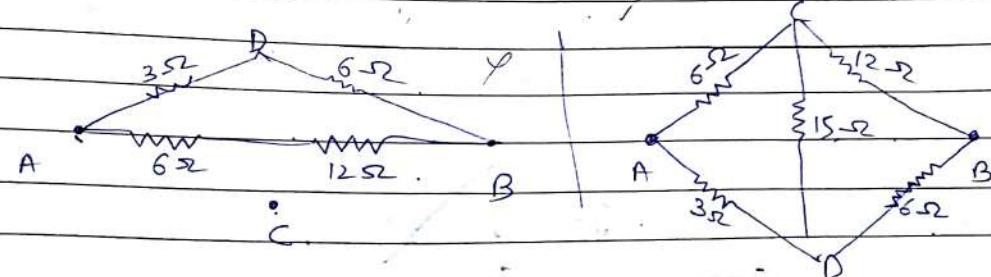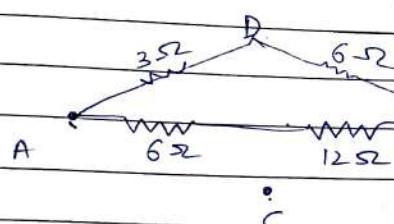

Yes it is balanced without stone bridge

$$\frac{6^2}{3} = \frac{12^2}{6}$$

no junction resistance wire logak

junction ①


$$\frac{1}{R_{AB}} = \frac{1}{6+12} + \frac{1}{3+6}$$

$$= \frac{6 \times 3}{6+3} + \frac{12 \times 6}{12+6}$$

$$= 6 \Omega$$

$$R_{AB} = 6 \Omega$$

(Q.)

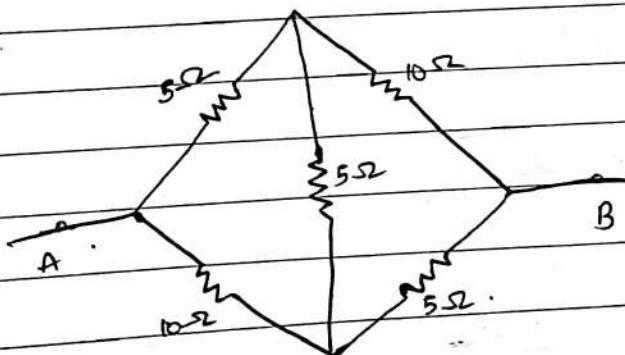


find equivalent resistance across A & B

It is not a simple bridge  
S.N.Q. 60+3

current will flow  $C \rightarrow D$  if battery attached  
we don't know abt which is series or in parallel

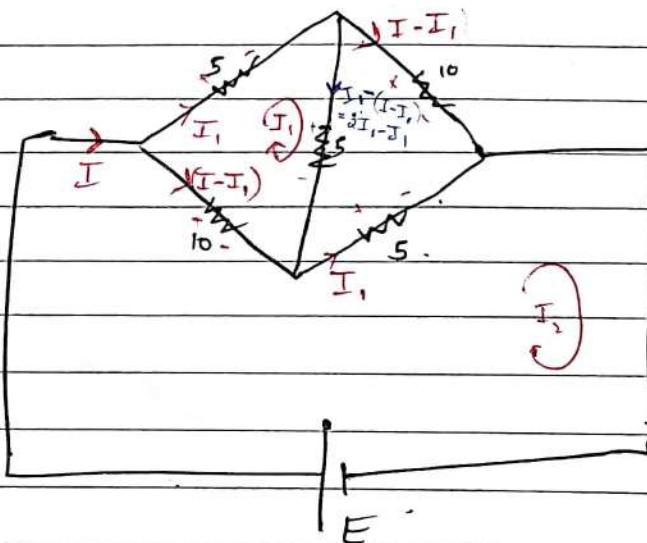thus add a battery b/w A & B of EMF  $\frac{E}{2}$



ab gr 2 loop  
not h o ob

hi  
h

$$\text{Req} = \frac{E}{I}$$

using KVL in loop ①


$$-5I_1 - 5(2I - I_1) + 10(I - I_1) = 0 \quad \text{--- (1)}$$

KVL  
in loop ②

$$-10(I - I_1) - 5I_1 + E = 0 \quad \text{--- (2)}$$

from ① & ②  $\frac{E}{I} = 7$  we get Req. Thus 7 ohms

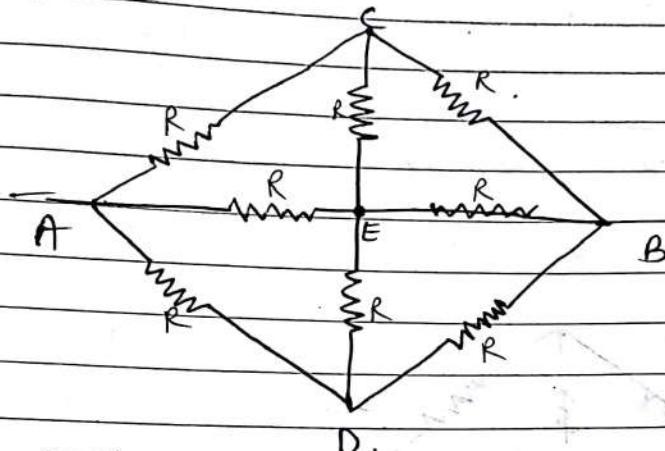
Calculation of equivalent resistance in a symmetrical circuit



Equivalent resistance across A & B

$$V_C = V_B$$

Now yeh dono analog mili ho yehek hi ho

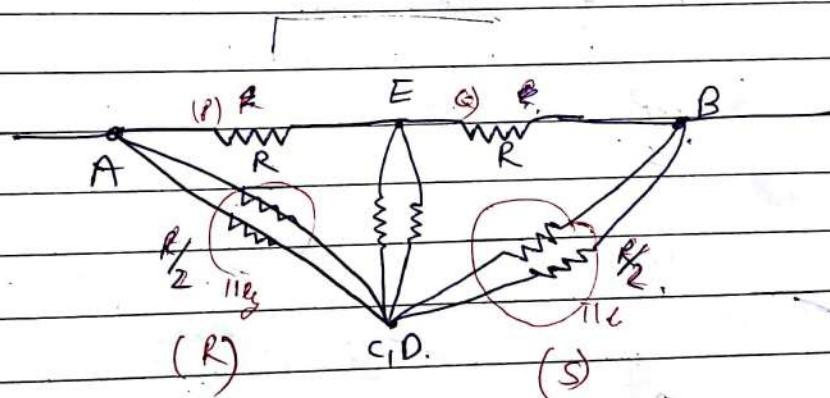


$$\frac{(P)}{(Q)} = \frac{(R)}{(S)}$$

$$V_E = V_C = V_B$$

The both are

equal  
to same

$2R + 2R$

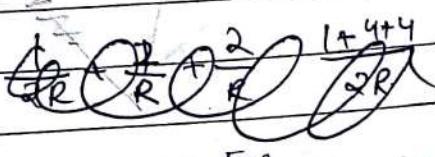


$\times 2$



DPP-21 CI  $\rightarrow$  Ex 1 Part I Part II Part III  
 $R_1 - R_2$  now also full Math 1  
 $2$

$$R = \frac{2R \cdot R}{2R + R} \\ = \frac{2R}{3}$$

$$\frac{1}{R_{AB}} = \frac{1}{2R} + \frac{1}{R} \\ \frac{1}{R_{AB}} = \frac{2R}{3}$$

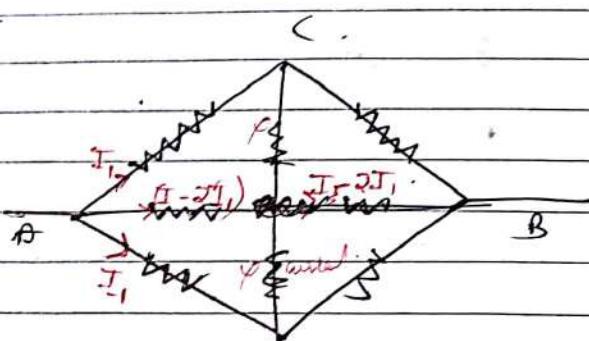majaria II

at end we know the  
all three  
will  
have  
some  
current  
ECD  
bar is  
broken

$$\frac{1}{R_{AB}} = \frac{1}{2R} + \frac{1}{2R} + \frac{1}{2R}$$

$$= \frac{2R}{3}$$


majaria

equipotentialism

mirroring



impedimental some

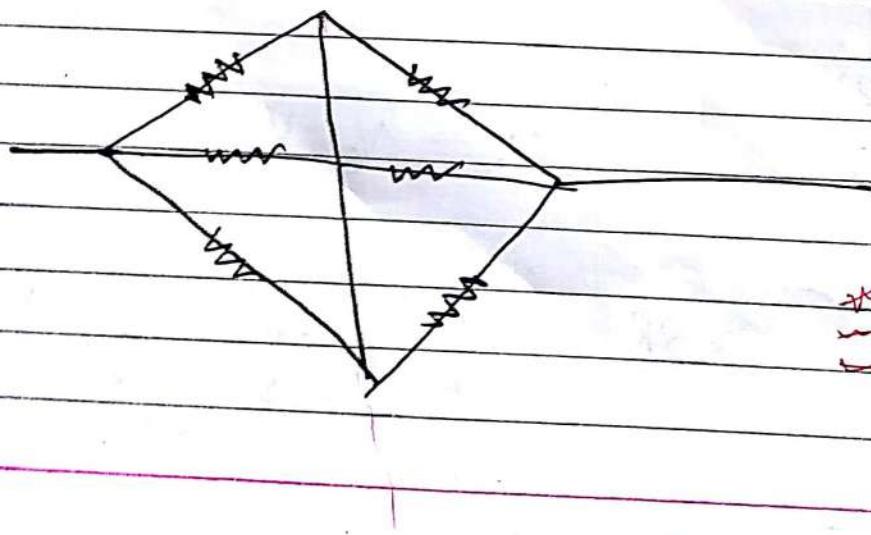

$\rightarrow$  at  $R'$   $\left| \begin{array}{c} \rightarrow \\ \leftarrow \end{array} \right| \begin{array}{c} \rightarrow \\ \leftarrow \end{array}$   
 $\rightarrow$  at  $R'$

mirrors



Circuit (2)

$$R_{AB} = 2R'$$

(1)

now  
they are  
parallel.


D E junction

$$\frac{R'}{3} = \frac{R}{3}$$


(2)

from (1) &amp; (2)

$$\frac{2R}{3}$$

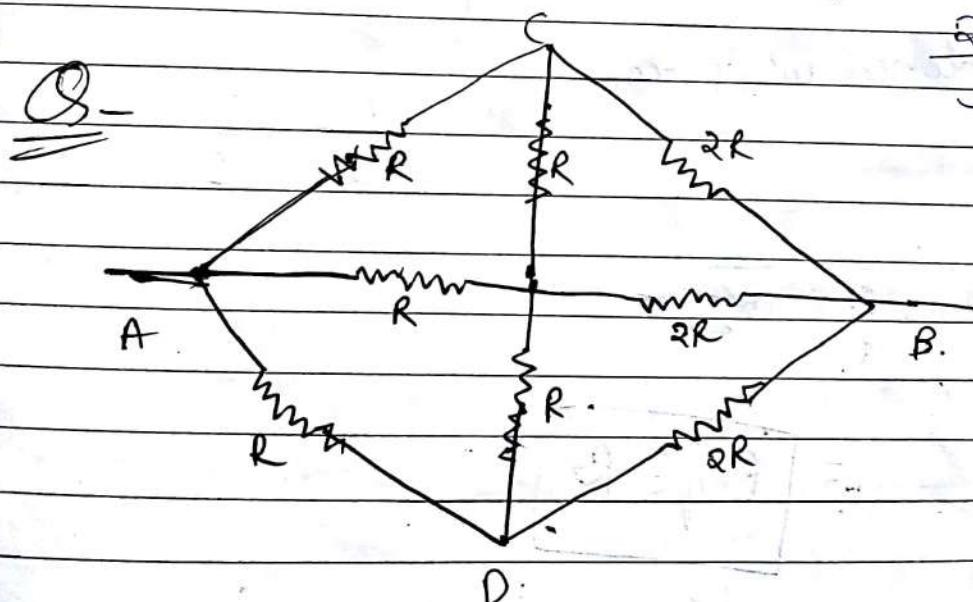


Calculate resistance  
across AB

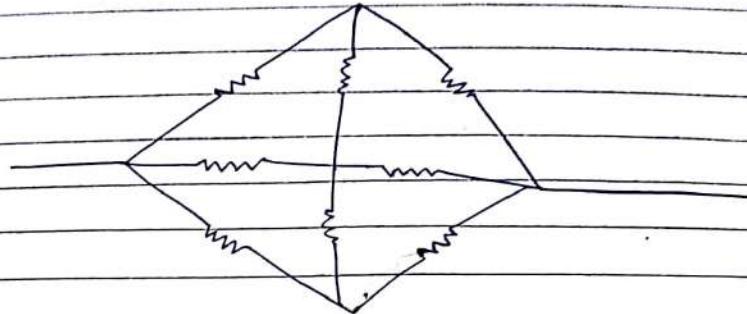

Due to symmetry  
pt C & pt D same.

$R = QR$  for  
 $R = QR$  middle ek jaisi

$3R$

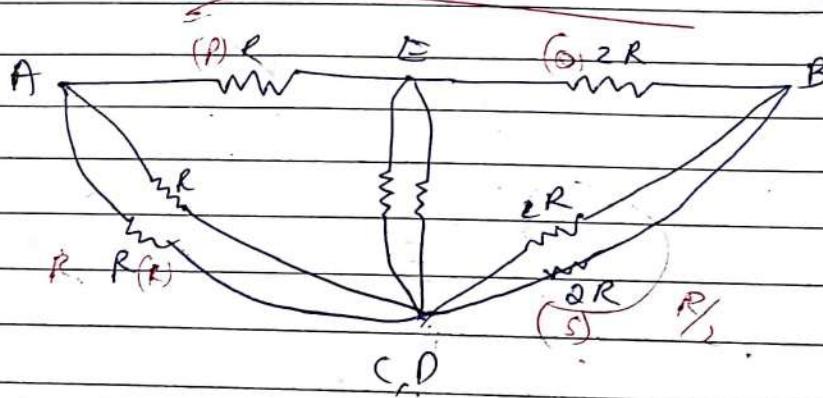


balanced wheel stone

$$\frac{P}{Q} = \frac{R}{S}$$

$$\frac{1}{R_{eq}} = \frac{1}{3R} + \frac{1}{3R/2}$$


$$= R_{eq} = R$$

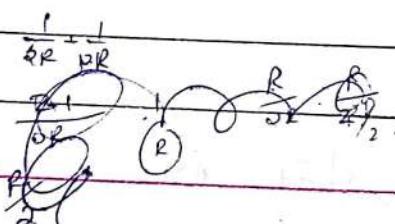


**icon** ✓

Date: 11  
Page No.  $\frac{2}{R} + \frac{1}{R} + \frac{1}{R}$


Q

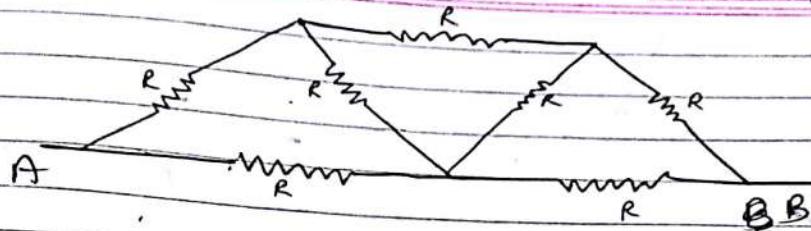

missed image

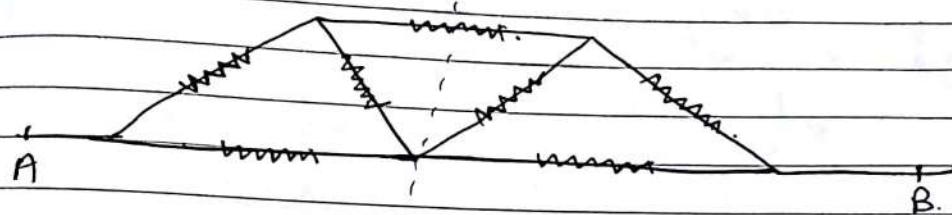


equivalence

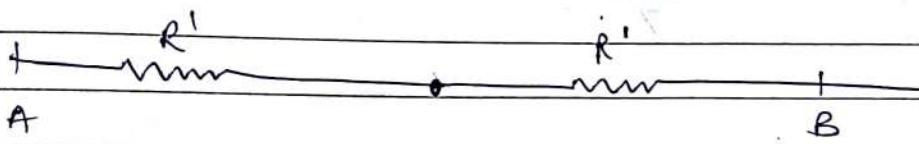


$$R_{AB} = 2R'$$

now to aim find  $R'$

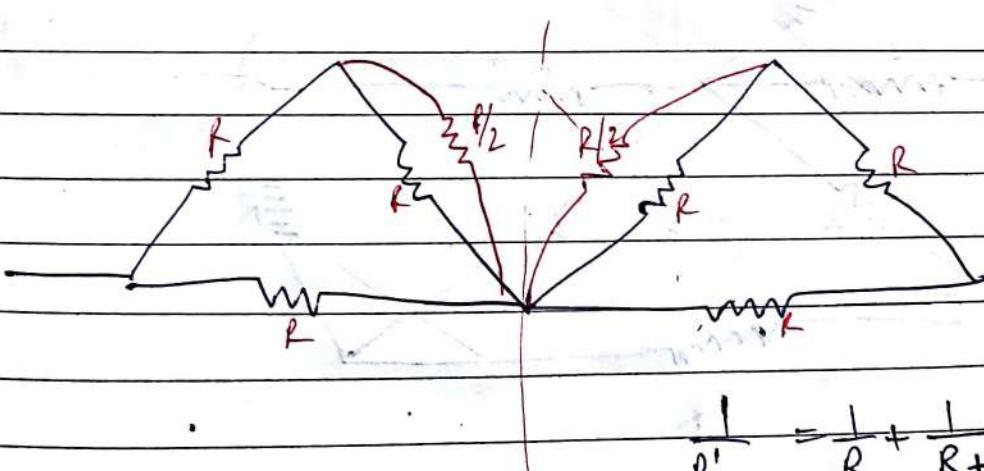

$$\frac{1}{R'} = \frac{1}{R} + \frac{1}{R+R/3} \Rightarrow R' = \frac{4R}{7}$$

$$\text{thus } R_{AB} = \frac{8R}{7}$$

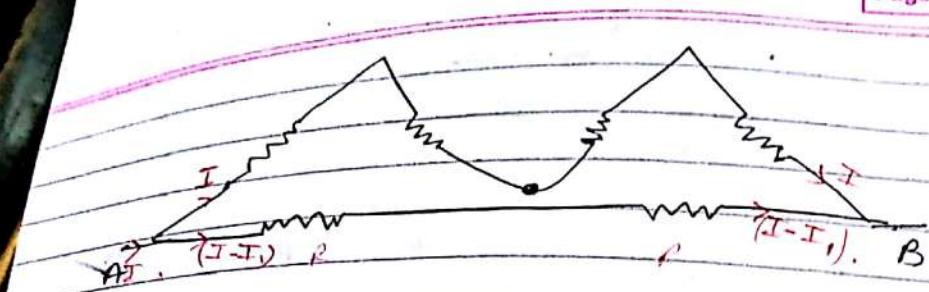

$$\frac{1}{R_{\text{eq}}} = \frac{1}{2R} + \frac{1}{2R + \frac{R}{3}}$$

left right middle


$$\frac{1}{2R} + \frac{1}{\frac{6R+R}{3}} = \frac{1}{2R} + \frac{3}{8R}$$


$$= \frac{4+3}{8R}$$

$$= \frac{7}{8R}$$

$$R_{\text{eq}} = \frac{8R}{7}$$

Q:-

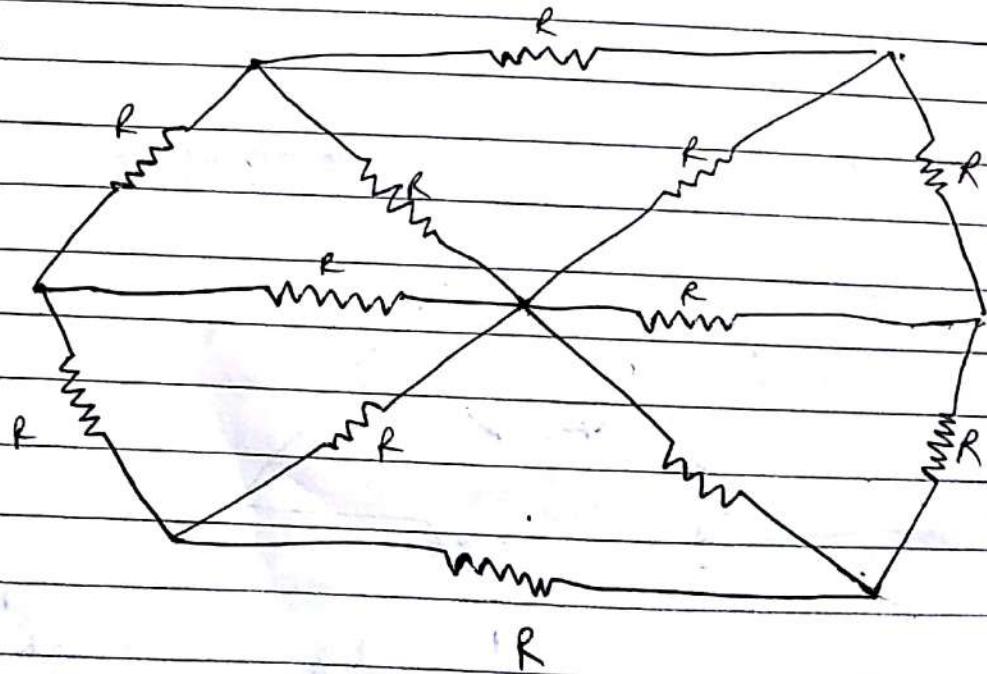


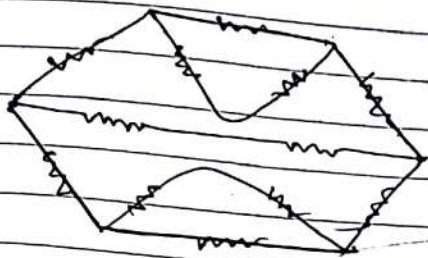


$$\frac{1}{R_{AV}} = \frac{2}{\frac{\alpha R + 2R}{3}} + \frac{1}{2R}$$

$$\frac{4R}{5}$$

or by connection removal method

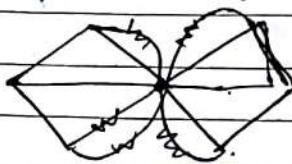

Q-

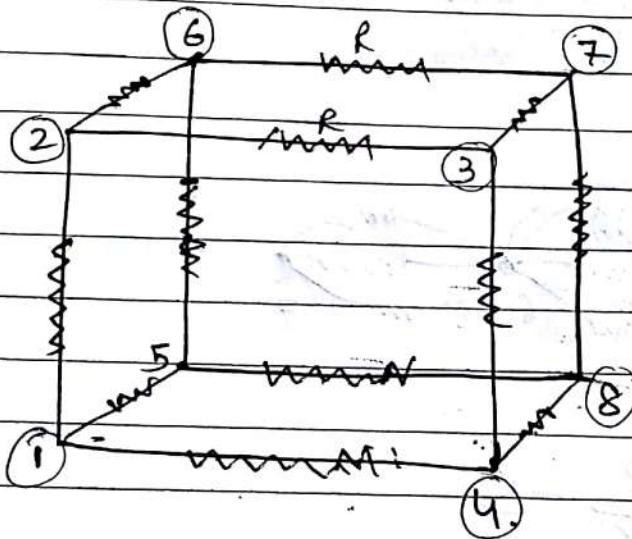

find equivalent resistance

- 1) across 1-4-7
- 2) across 1-2-3
- 3) across 1-2-4


$$\frac{\frac{1}{\alpha R} + \frac{1}{R}}{2R} \cdot \frac{3}{2R}$$



$$\frac{2R}{3}$$

$$\frac{8R}{3} \cdot \frac{2R + 2R + R + R}{3} \cdot \frac{3}{6R + 2R \cdot 3}$$


$$\frac{2R + R + R}{3}$$

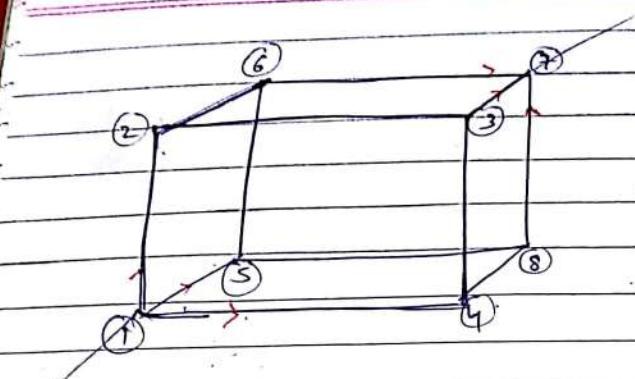


due to boundary:

2      6  
5      3  
4      1  
8      8

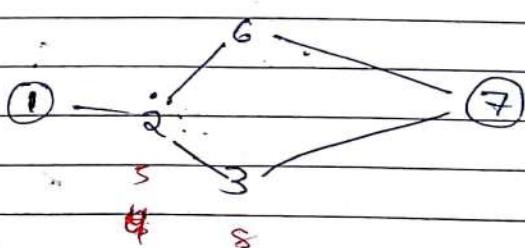Potential      Potential  
some            some



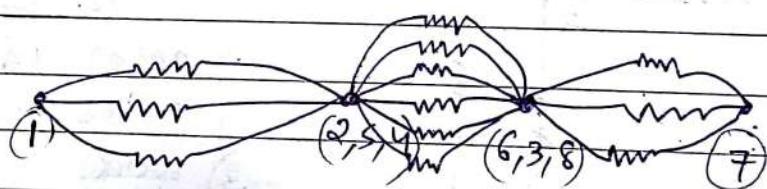
2, 5, 4.  $\rightarrow$  some potential  
6, 3, 8  $\rightarrow$  some potential




$$R_n = \frac{R}{3} + \frac{R}{6} + \frac{R}{3}$$

$$= \frac{5R}{6} \text{ Ans.}$$


2) 1 &amp; 3.

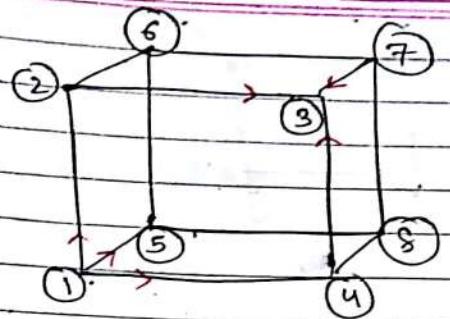

due to Sym.

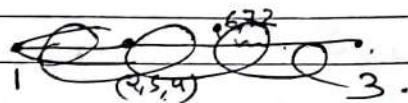 $2, 4 \rightarrow$  some potential $6, 8 \rightarrow$  some potential  $R/2$ 

res-

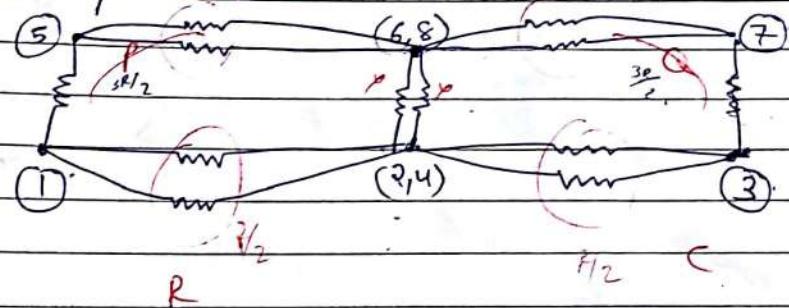

$$\text{Ind}(2,6) \text{ & } (4,8)$$

in  $\frac{1}{2}$  &  $\frac{1}{2}$  T arm.


so no current flow.

(fallt)

$$\frac{P}{Q} = \frac{R}{S}$$

balanced Wheatstone bridge
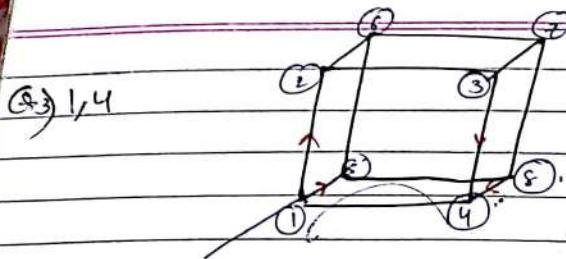
$$R_{13} = \frac{3R \cdot R}{3R + R} = \frac{3R}{4}$$




due to sym,

2-5 same potential

3-8 same potential

(Ans)


4.

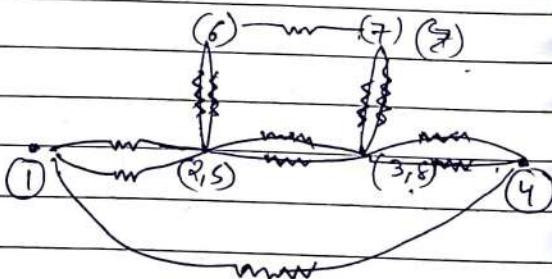

$$R_{14} = \frac{7R}{12}$$

$$R + \frac{1}{R}$$
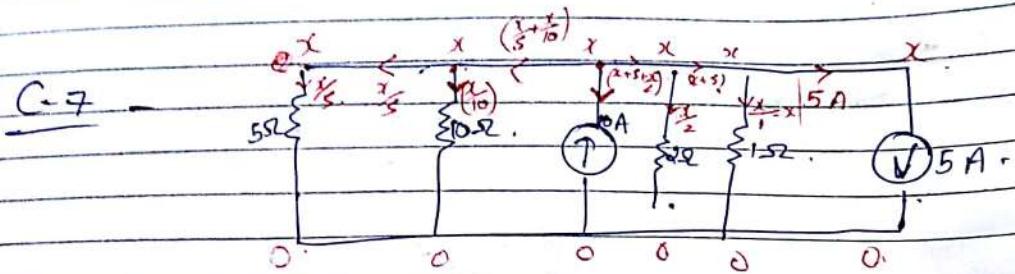
$$\begin{aligned} & \frac{\frac{1}{R} + \frac{1}{R}}{2R} + R + \frac{1}{R} + \frac{1}{R} \\ & \frac{1}{2R} + \frac{1}{R} + \frac{1}{R} + R + \frac{1}{R} + \frac{1}{R} \\ & \frac{1}{2R} + \frac{1}{R} + \frac{1}{R} + R + \frac{1}{R} + \frac{1}{R} \end{aligned}$$




$$\frac{x}{5} + \frac{x}{10} + 10 + \frac{x+5+x}{10} = 0$$

$$(2x + x + 100 + 10) + 10 + 5x = 0$$

$$15x + 110 = 0$$
 ~~$18x + 150 = 0$~~ 
 ~~$x = -150$~~ 
 ~~$x = 10$~~

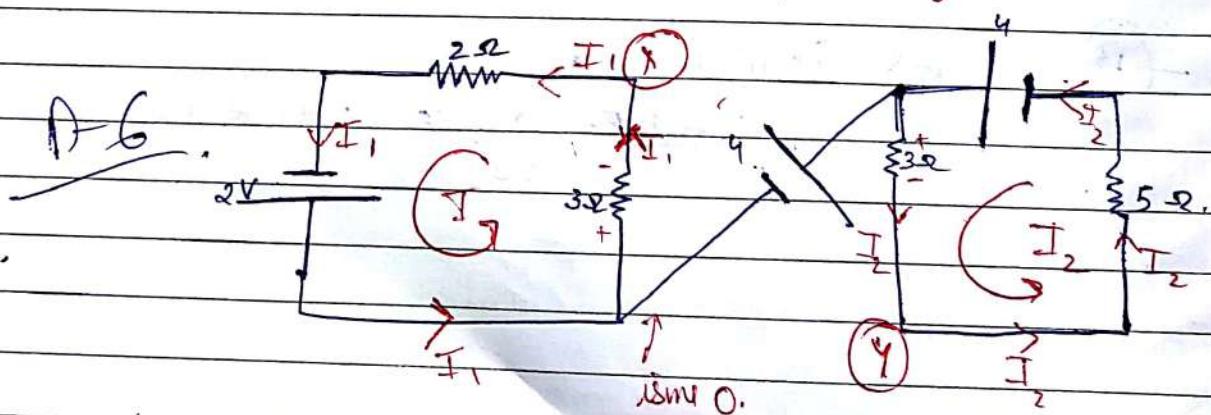C-10  $V_S = V_A - V_B$  ~~2-yoh~~ battery band



$$I_1 = \frac{2}{5\Omega + 3}$$

$$I_2 = \frac{4}{3+5} = 1$$

$$V_x + 3I_1 + 4 - 3I_2 = V_y$$

$$V_x - V_y = 3I_2 - 3I_1 - 4.$$

$$3\frac{1}{2} - 3\frac{2}{5} - 4$$

$$\frac{3}{2} - \frac{6}{5} - 4$$

$$\frac{15 - 12 - 40}{10}$$


$$= \frac{-37}{10}$$

no effect b/c both come in one current nli. he  
indcpn of internal resistance

$$\text{D-9} - AC = 2000 \text{ Aul: } 500$$


$$\therefore BC = 1500$$
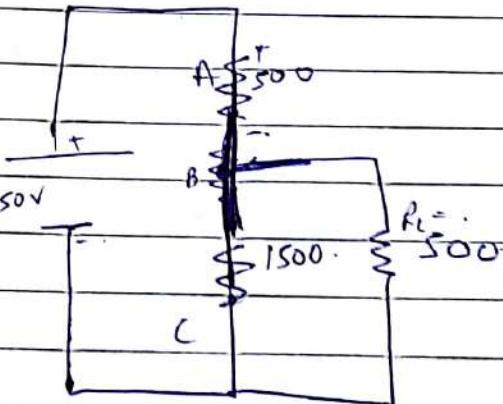
$$I = \frac{50}{500 + \frac{1500 \times 500}{1500 + 500}}$$



$$\text{then } V_1 + V_2 = V$$

10)

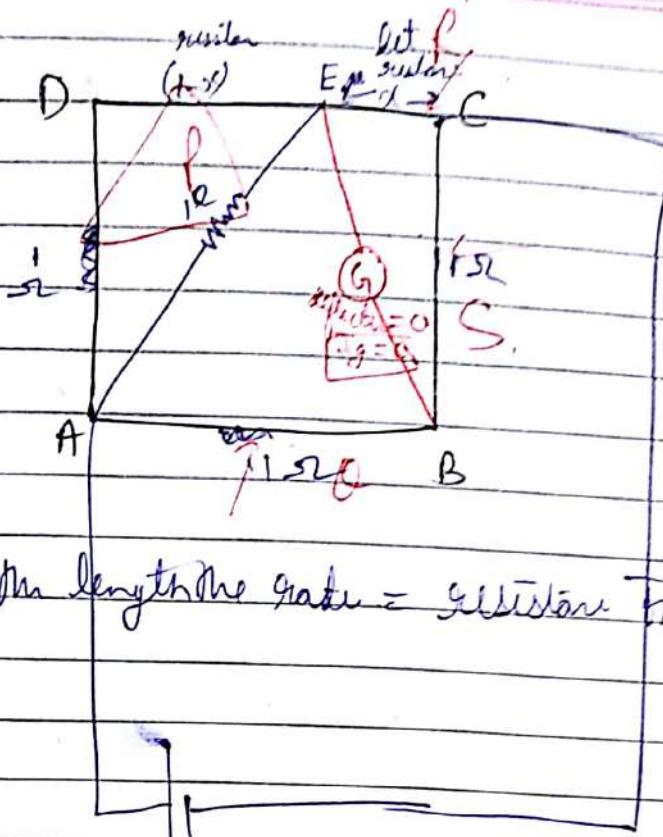

The length of the gate = distance of gate.

$E, B$  both parallel.

$$\rho = \frac{2-x}{2-x+1} = \frac{2-x}{3-x} \cdot \frac{l}{a} = \frac{r}{s}$$

$$\frac{2-x}{3-x} = \frac{x}{1}$$

$$\frac{x-2}{x-3} = x$$

$$x^2 - 3x = x - 2$$

$$x^2 - 4x + 2 = 0$$


$$(x-2)(x-1)$$

$$(x-2) = x(x-3)$$

$$x = -$$


$$\frac{CE}{ED} = \frac{x}{(1-x)}$$

length of section of the gate

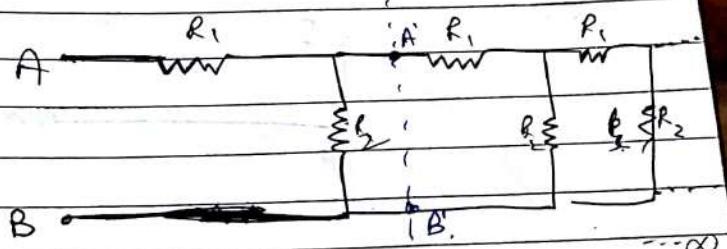Combination of cellInfinite network

equivalent across A & B let R.


from A to B' its also R.

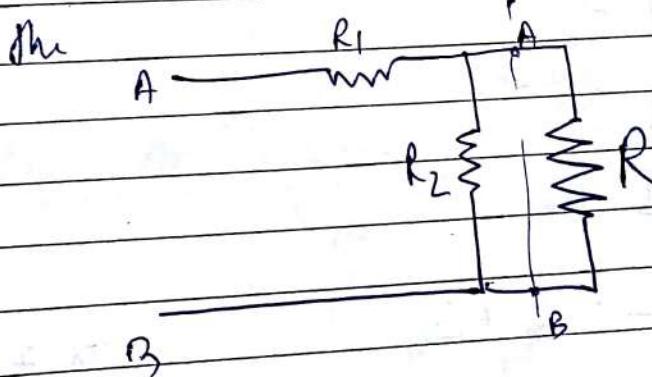

$$\frac{R_2 R}{R_2 + R} + R_1 = R$$

## Combination of cells:

Series

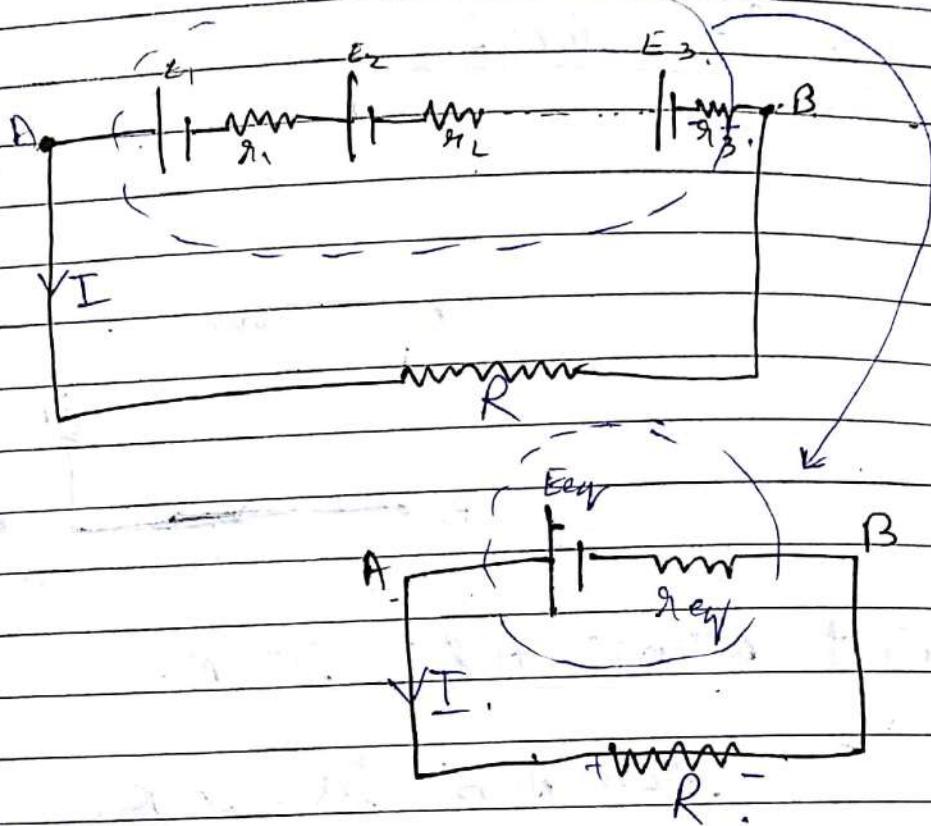

$$I = \frac{E_{eq\ total}}{R + R_{eq}}$$

$E_{eq}$  : total emf

①

using KVL in fig ①

$$-IR - IR_n + E_{eq} \dots \text{eq 1st cell}$$

$$I = \frac{E_1 + E_2 + \dots + E_n}{R + R_1 + R_2 + \dots + R_n}$$


②

$$E_{eq} = E_1 + E_2 + E_3 + \dots + E_n$$

$$R_{eq} = R_1 + R_2 + R_3 + \dots + R_n$$

$$\text{if } E_1 = E_2 = \dots = E \\ \text{and } R_1 = R_2 = \dots = R$$


$$I_{eq} = \frac{nE}{R + nR}$$

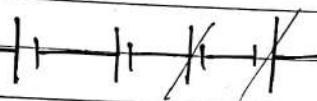

→ If  $m$  cells are connected with opposite polarity then:

$$I_{eq} = \frac{(n - 2m)E}{R + mR}$$

### Parallel Combination

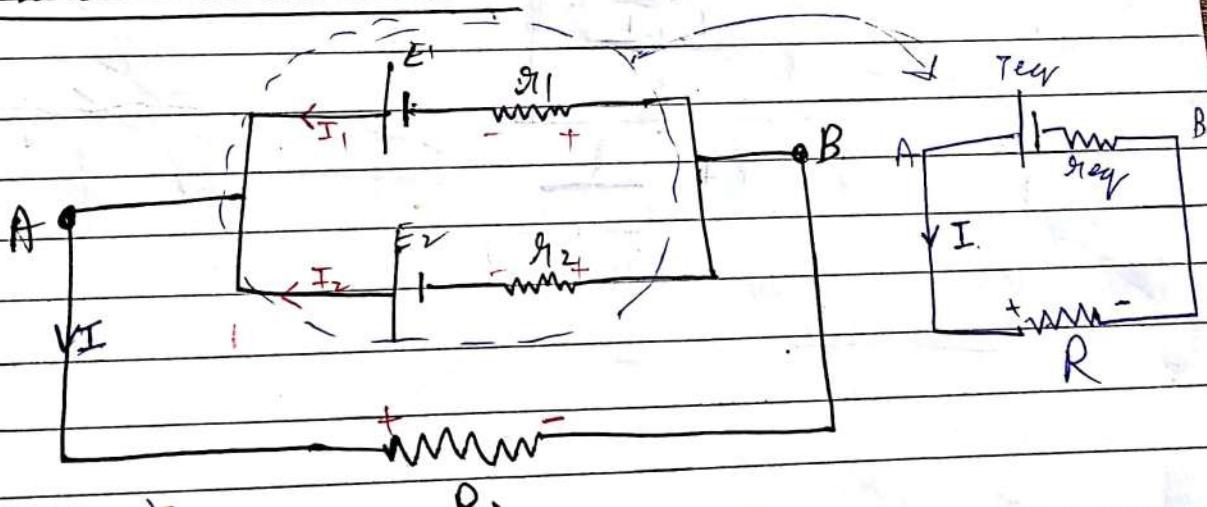

$$\left( \frac{1}{R_1} + \frac{1}{R_2} \right)^{-1}$$

$$E_{eq} = \frac{E_1}{R_1} + \frac{E_2}{R_2}$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

$$I = \frac{E_{\text{eq}}}{R + r_{\text{eq}}} \quad (1)$$

$$E_1 - I_1 r_1 = IR \quad \text{and} \quad E_2 - I_2 r_2 = IR$$

$$I = I_1 + I_2$$

$$I = \frac{E_1 - IR}{r_1} + \frac{E_2 - IR}{r_2}$$

$$I = \frac{r_2(E_1 - IR) + r_1(E_2 - IR)}{r_1 r_2}$$

$$I = \frac{E_1 - IR}{r_1} + \frac{E_2 - IR}{r_2}$$

$$= I \left( \frac{1}{R_1} + \frac{1}{R_2} \right) = \frac{E_1}{r_1} + \frac{E_2}{r_2}$$

$$\frac{E_1 - IR}{r_1} + \frac{E_2 - IR}{r_2}$$

$$I = \left\{ \frac{\frac{E_1}{r_1} + \frac{E_2}{r_2}}{\frac{1}{r_1} + \frac{1}{r_2}} \right\}$$

$$R + \frac{1}{\left( \frac{1}{r_1} + \frac{1}{r_2} \right)}$$

~~cancel~~

(2)



$$E_{eq} = \left( \frac{E_1}{R_1} + \frac{E_2}{R_2} \right)$$

$$\frac{1}{R_{eq}} = \frac{1}{R_1} + \frac{1}{R_2}$$

put  $E_1$  &  $E_2$  with polarities

$$\frac{1}{R_{eq}} \geq \frac{1}{R_1} + \frac{1}{R_2}$$

### Mixed grouping

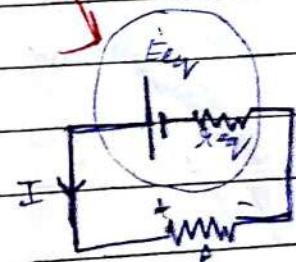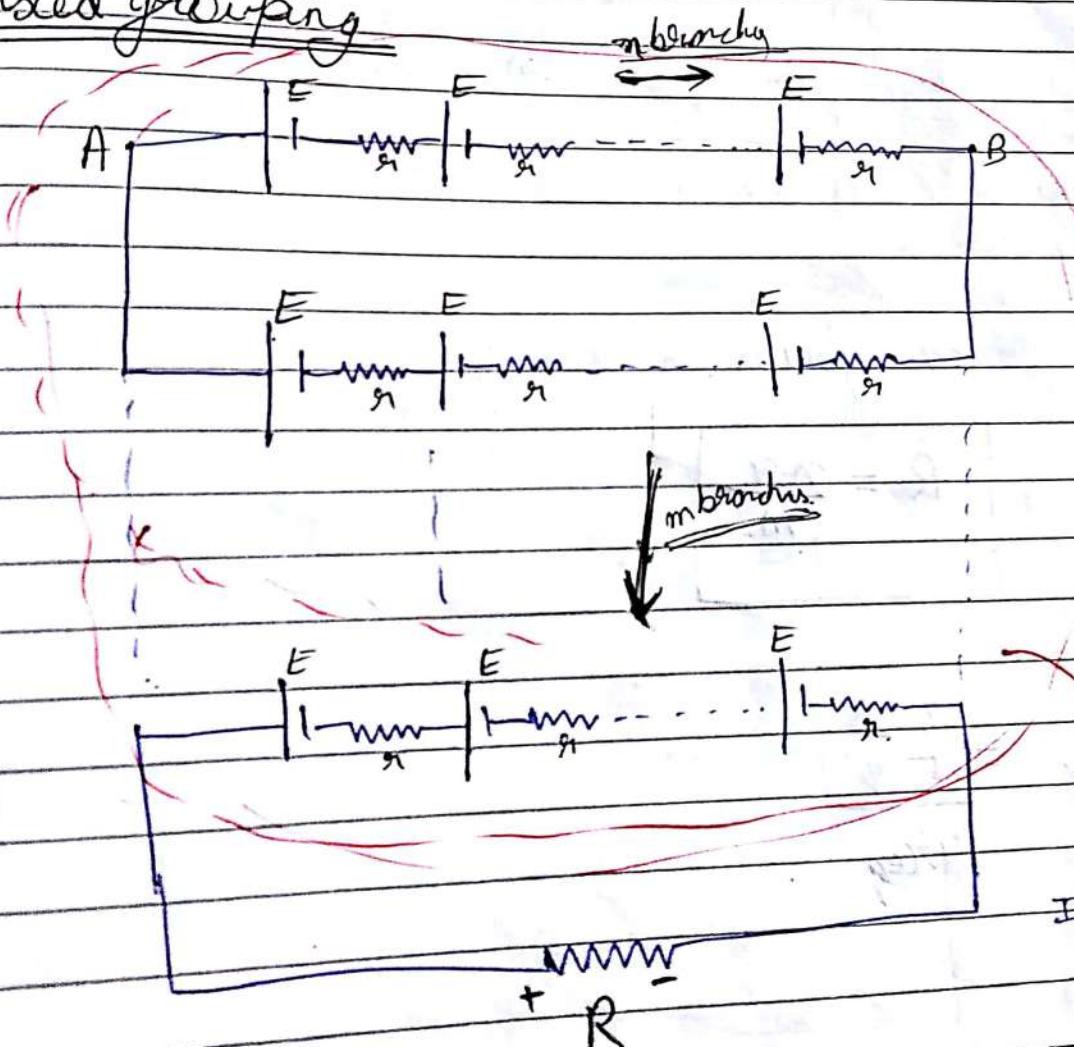

$$I = \frac{E_{eq}}{R + R_{eq}}$$

equivalent e.

nE

$$\text{equivalent Emf} = nE$$

$$E_{\text{eq}} = nE$$

$$r_{\text{eq}} = \frac{n r}{m}$$

$$T = \frac{nE}{(R + \frac{nR}{m})}$$


total no of cells m.n.

for max power in load R.

$$R = \frac{n r}{m}$$

$$P_{\text{max}} = \frac{E_{\text{eq}}^2}{4r_{\text{eq}}}$$

$$4r_{\text{eq}}$$

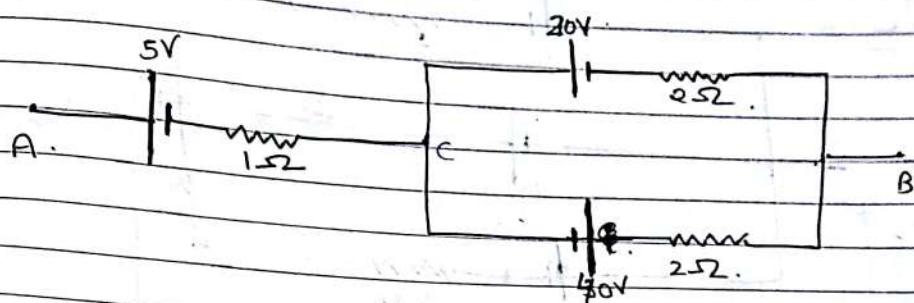Q.find  $E_{eq}$  &  $r_{eq}$ .

$$E_{eq} =$$



~~$$\frac{10}{2} + \frac{-10}{2}$$~~


~~$$E_{eq} = 10 - 10 = 0$$~~

$$E_{eq} = \frac{40 - 20}{2 + 2}$$

$$\frac{1}{2} + \frac{1}{2}$$

$$= 10V$$

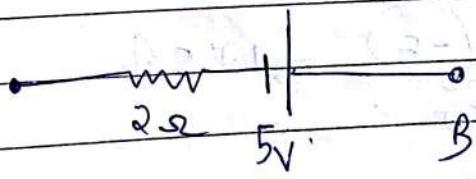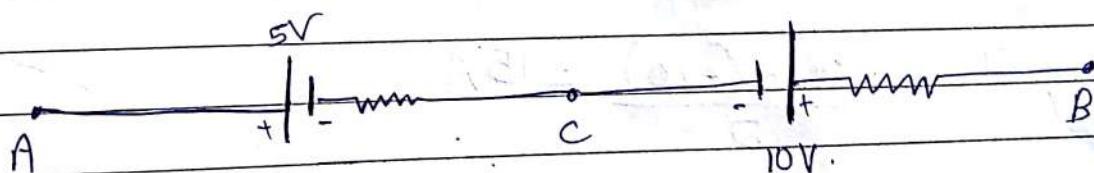

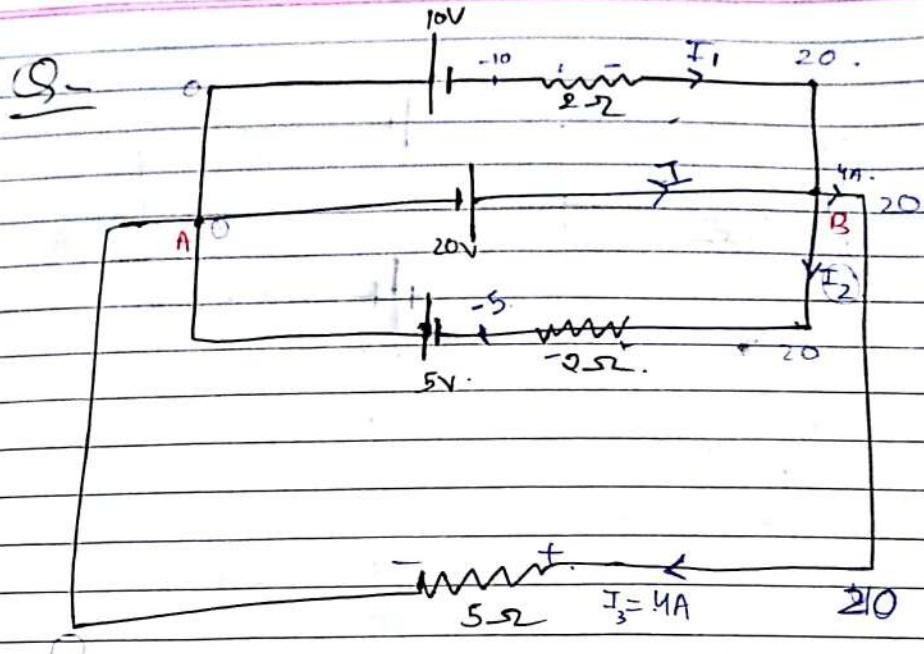

- Calculate  
 1) current flowing in  $5\ \Omega$  resistance.  
 2) current flowing through branch  
 of 20V battery

$$\text{Eqn} = \frac{\text{potential in } B \text{ branch} - 20}{5} = 15 \text{ A}$$

$\text{AB potential} = 11$   
 $\text{AG potential} = 11$


$$I_1 = \frac{20 - (-10)}{2} = 15 \text{ A}$$

$$I_2 = \frac{20 - (-5)}{2} = 12.5 \text{ A}$$

$$I = I_1 + I_2 + I_3 = 15 + 12.5 + 4 = 31.5 \text{ A}$$

## Electric instruments

### 1) Galvanometer

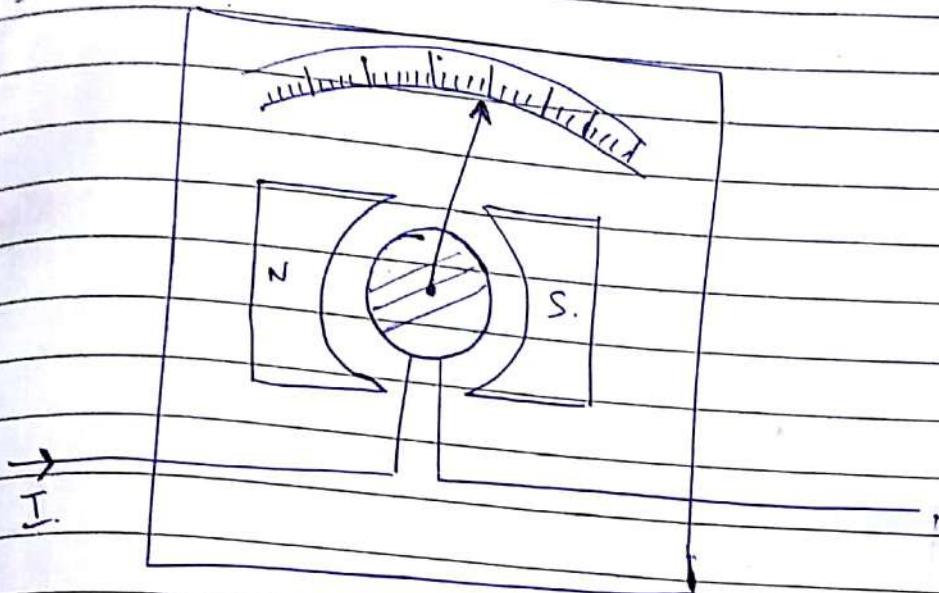

Due to magnetic field  
torque on MF.

$$\text{Torque} = BINA$$

↓      ↓      ↓      ↓  
 magnetic field      current      area of coil      no. of turns

$$\vec{\tau} = \vec{P} \times \vec{E}$$

$$\vec{\tau} = \vec{M} \times \vec{E}$$

$$M = NI A$$

magnetic dipole moment

$$T_{\text{spring}} = C\phi$$

$\epsilon \rightarrow$  torsional const  
 $\phi \rightarrow$  angle of deflection

at equilibrium

$$T_{\text{spring}} = T_{\text{magnetic field}}$$


$$C\phi = BINA$$

$$\boxed{\phi = \frac{BNA}{C} \cdot I}$$

$$\phi \propto I$$

angle of deflection  $\propto$  current

it is represented as

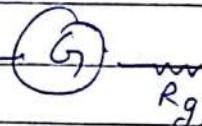

$I_g \rightarrow$  full scale deflection current


- Ammeter is always connected in series with element we want to measure if parallel then it will blow up

- Ammeter has very less resistance so it ~~disturb~~ <sup>does not</sup> the circuit
- Voltmeter is connected in parallel cause want to measure whole voltage across ammeter

~~• voltmeter is connected in || it has a very large resistance if it will have less than 100 ohms then it will affect the circuit that's why that part is false~~

galvanometer  
 galvano meter  
 Ammeter  
 Ammeter to current to be measured  
 calculate current  
 Date: / /  
 Page No. / /

Ammeter -

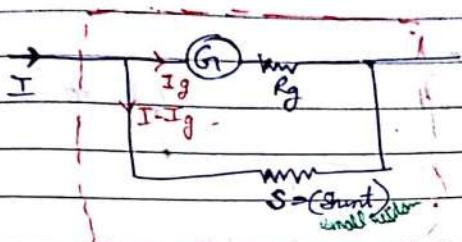

$I \rightarrow$  range of ammeter  
 (max current can be measured)

if voltage across  $R_g$  &  $S$  is equal

$$I_g R_g = (I - I_g)S$$

$$S = \frac{I_g R_g}{(I - I_g)}$$

$$\frac{1}{R_{\text{eff}}} = \frac{1}{R_g} + \frac{1}{S}$$

(A) now  
 $R_a$  = resistance of ammeter

eq resistance of shunt & galvanometer


$$R_a = \frac{R_g \times S}{R_g + S}$$

$$Z = \frac{I}{0.015 + R}$$

if  $R_g \gg S$

$$R_a \approx S$$

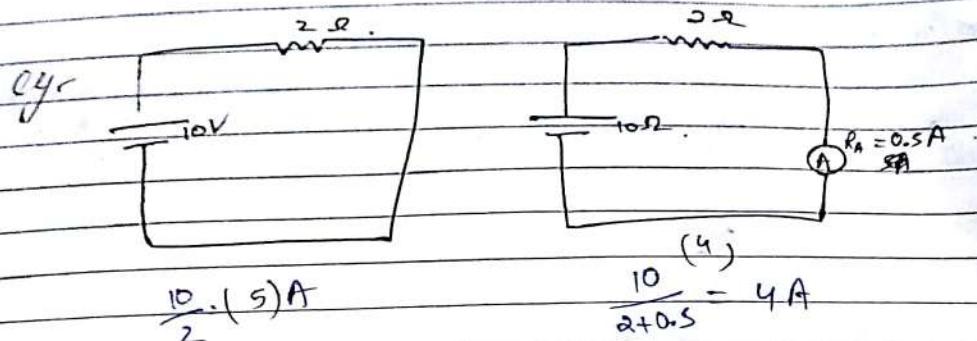
To measure the current  $\text{---} A \text{---}$  is connected with series in that branch



∴ change in current

Now we can get found reading by taking account of  
ammeters = 0

Q find reading of Ammeter

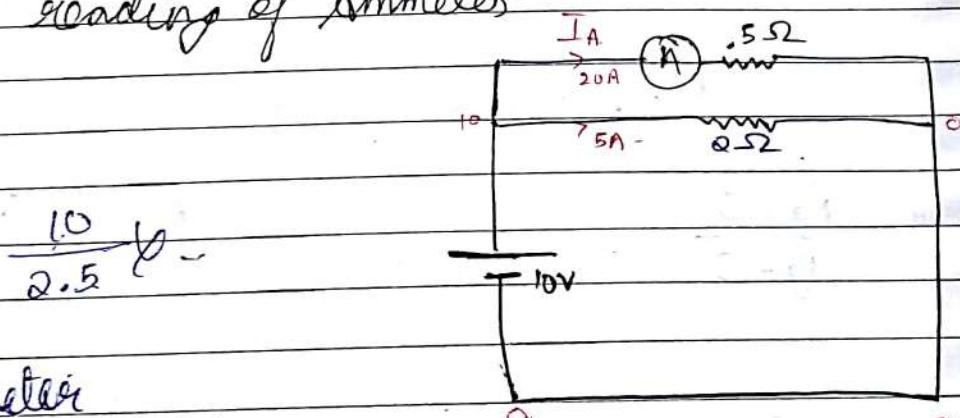

in another

$$= \frac{10}{0.5} = 20$$

$$I_A = \frac{10-0}{0.5} = 20A$$

only in that branch

net — in an electric circuit —  $\textcircled{A}$  — is treated as resistor

$$V = I_g(R_g + R)$$


$$\frac{V - R_g}{I_g}$$

iron

Date: / /  
Page No.
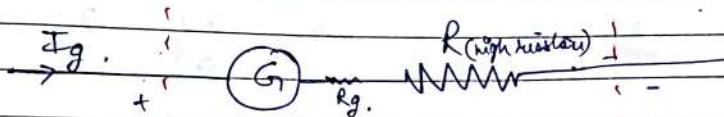
### Voltmeter

It measures potential difference across any two points in electrical circuit.



$$V$$

$V \rightarrow$  range of voltmeter  
 $R \rightarrow$  high resistance  
 $R_g \rightarrow$  galvanometer resistance

high resistance is connected with (G) in series to make it Voltmeter

$$V = I_g(R_g + R)$$


$$R = \frac{V}{I_g} - R_g$$

To calculate potential diff  $\textcircled{1}$  is connected in ||

series  $\textcircled{1}$   $\textcircled{2}$   $\textcircled{3}$

$$R_V = R_g + R$$


$$R_V = R \quad \text{if } R_g \ll R$$

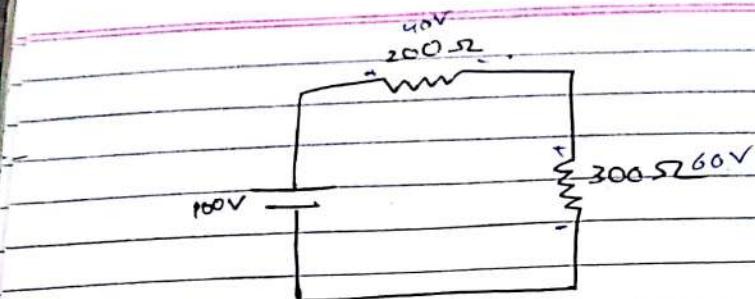

$$V = IR$$

$$\frac{100}{500} \times 200 = 40$$
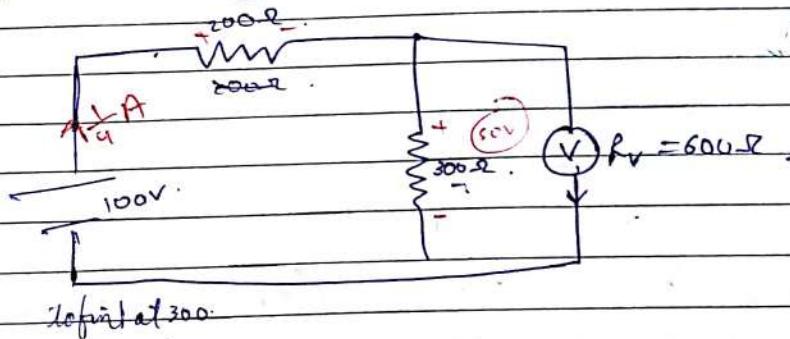
$$V = \frac{100 \times 300}{500 \times 200} = 60$$



Reading of Voltmeter = Potential diff across terminals of Voltmeter

& - (V) - is comm in 11 but resistors series in path 10.

$$\frac{1}{300} + \frac{1}{600} = \frac{2+1}{600} = \frac{3}{600} = 0.005$$

now they are seen

400 ohm

$$V = IR$$

$$\frac{100}{400} = I$$

we get 0.25

but from prev it was 60.

$$\frac{1 \times 600}{4}$$

$$\frac{1}{4} \times 600$$

$$\frac{150}{600}$$

Volt - consumed a little current  
 Then we consume power. Current change kardia use hame

wall consequences ka gadi kya ha - (v) galt nahi tho


If we want load loading

This it should be ideal so resistors of  $\sim 0\Omega$  is  $\rightarrow$   
 Then it doesn't withdraw current

In a circuit voltmeter is treated as resistor.
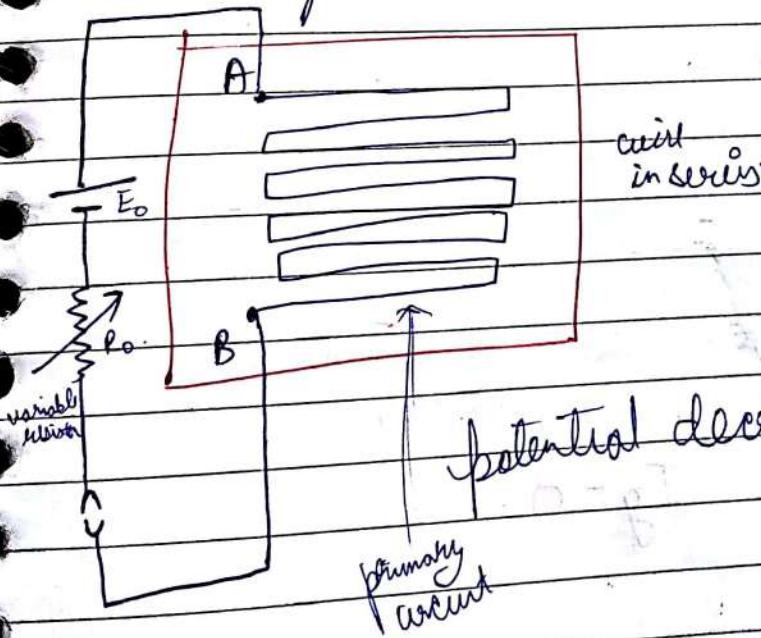
### Potentiometer (ideal voltmeter junction notation)

It measures potential difference across any two points in circuit.



uniform wire AB length-L  
 resistance,  $= R$

potential decreases uniformly b/c wire is uniform

$$\frac{V_B}{V_F + G_F}$$

current

$$(I_o = \frac{E_0}{E+R_0})$$

potential drop across potential meter.


$$V_A - V_B = I_o R$$

$$\left( \frac{E_0}{E+R_0} \right) R$$

Potential gradient


change in potential per unit length

$$R = \frac{V_A - V_B}{l}$$

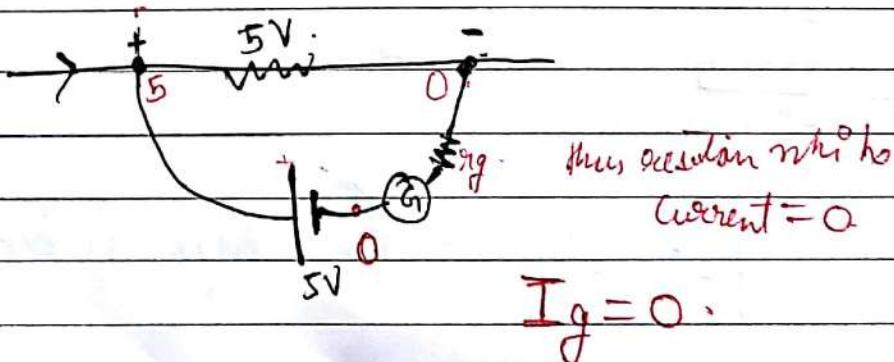Concept

Standardisation

Isolate the process of finding potential gradient of potentiometer wire with the help of cell of known known emf

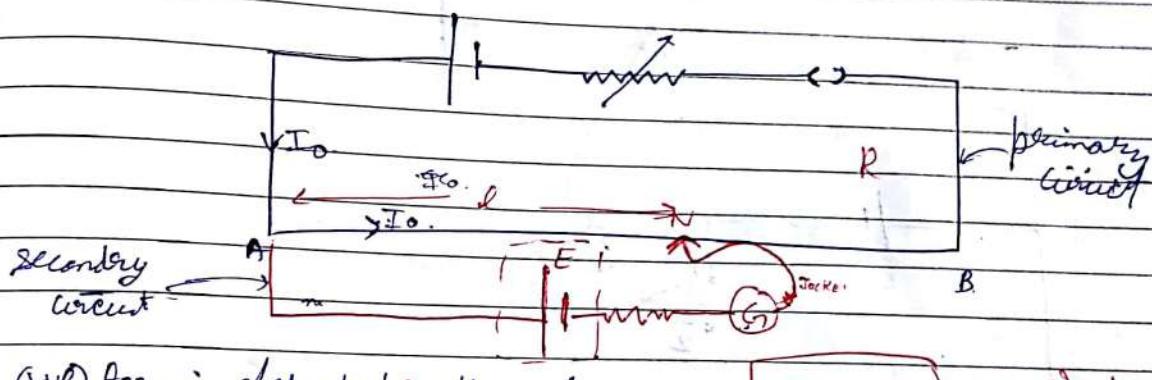Circuit diag.

When null pt is obtained when current in (G) branch becomes 0  
dis of null pt is l.


now potential across A & N is the emf of Standard cell.

permitt length K charge

Total charge KL

$$E = Kl$$

## Comparison of emf of two Cells

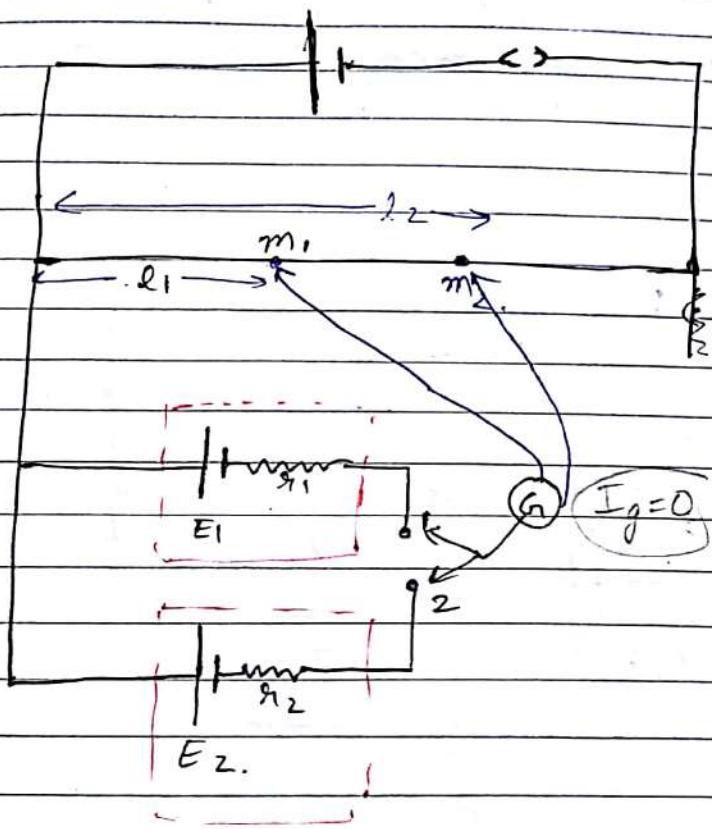


position - 1


$$E_1 = Kl_1$$

$$E_2 = Kl_2$$

$$\frac{E_1}{E_2} = \frac{l_1}{l_2}$$

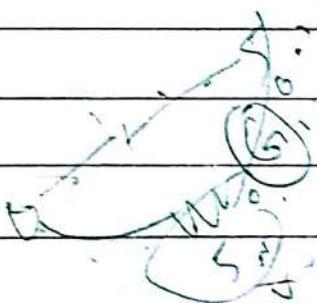

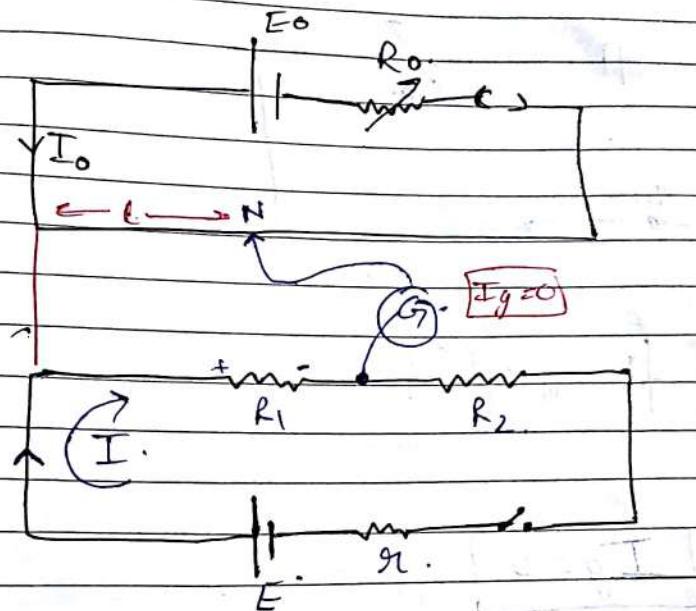Calculation of current in a resistance if its resistance is known.



null point


$$I_g = 0$$

pot diff across  $R_1$  = pot diff across A & B.

$$IR_1 = Rl$$

$$I = \frac{Rl}{R_1}$$

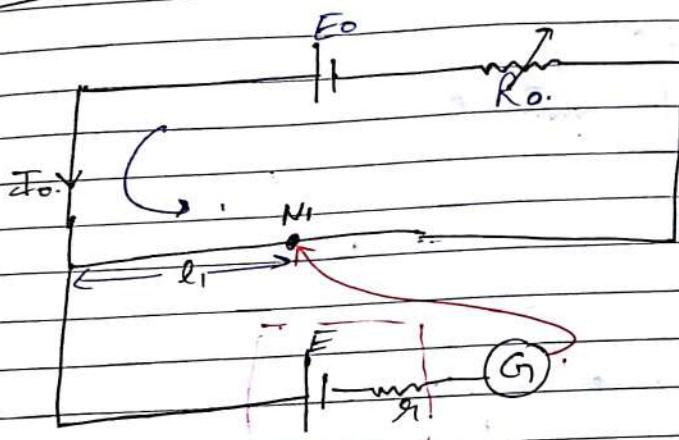
## Calculation of internal resistance of a Cell



mid point

$$I_g = 0$$

$$E = k l_1 \quad \text{--- (1)}$$

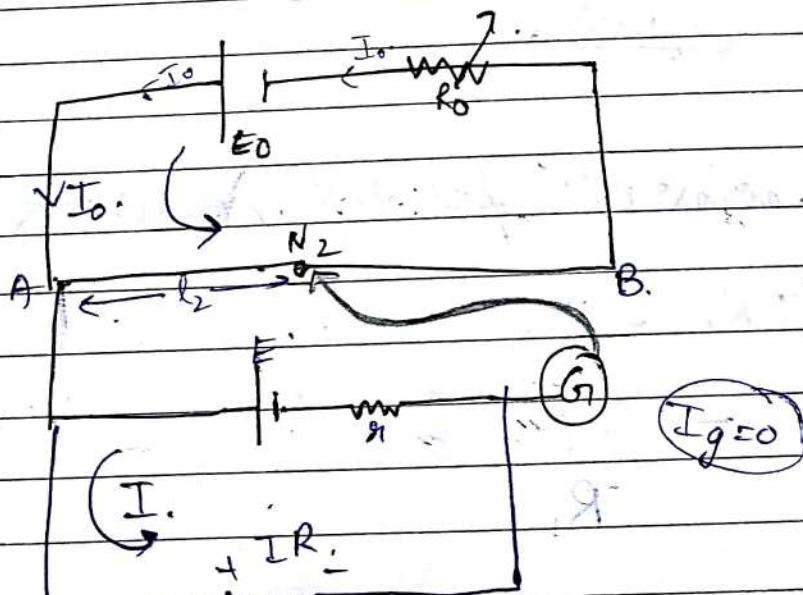

$R$  (known)

$$(VI) \text{ os } IR = l_2$$

$$\left( \frac{E}{R+r} \right) R = kl_2 \quad \text{--- (2)}$$

Solving eq (1) & (2)

$$r = \frac{(l_1 - l_2) R}{l_2}$$


internal resistance

max P.D. which can be measured by potentiometer wire is the potential diff across potentiometer wire.

Potentiometer does not draw any current from secondary circuit while measuring potential diff. That's why it's known as ideal.

$\rightarrow AB \rightarrow \text{max potential}$

ideal.

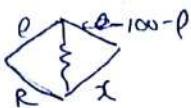


iron


Date: / /  
Page No.
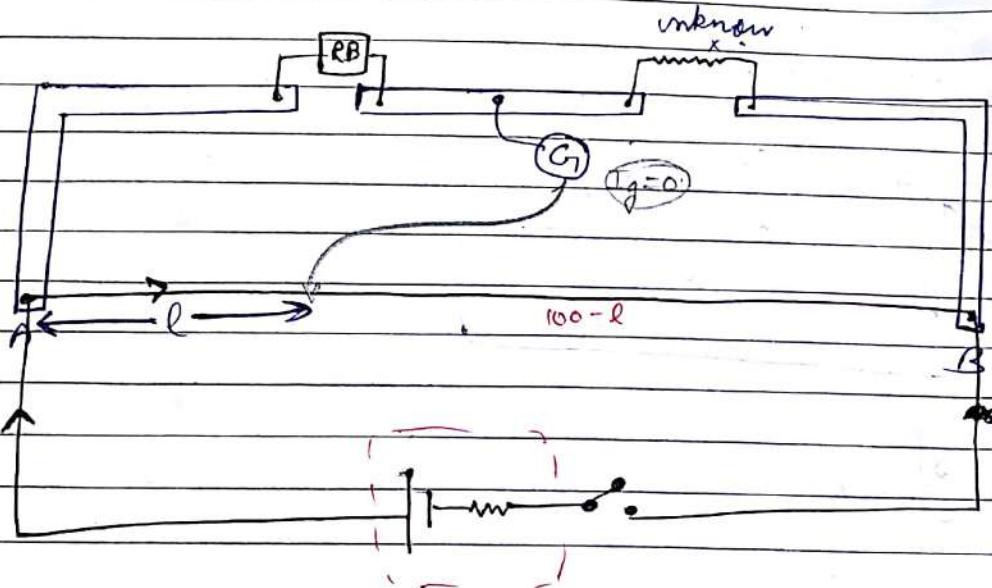
## Meter bridge


It has 1 m long wire and works on the principle of Wheatstone bridge.



$$AB = 1 \text{ m}$$

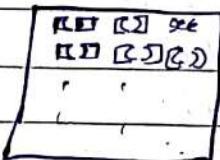

Resistance box

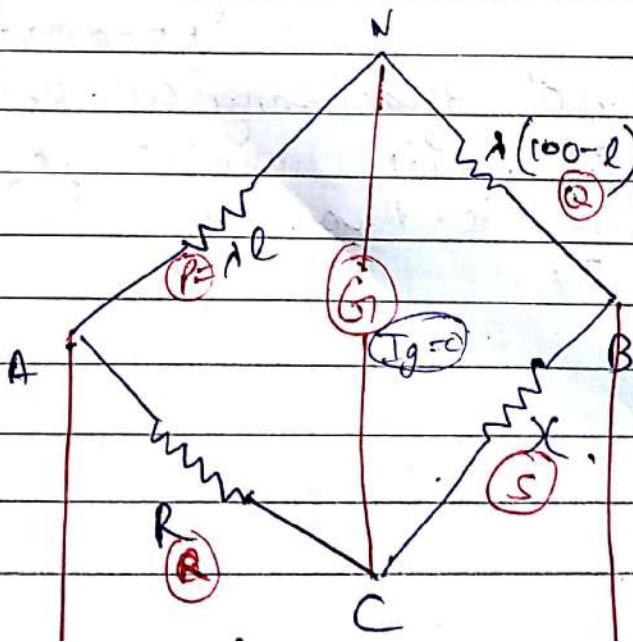

$$\frac{P}{Q} = \frac{R}{S}$$


$$\frac{l \cdot l}{100 - l} = \frac{R}{S}$$

$P = R(100 - l)$   
 $Q = l$



icon

Date: / /  
 Page No.

$$X = \frac{R(100 - l)}{l}$$

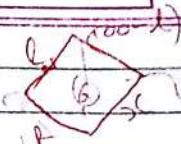

Post office box

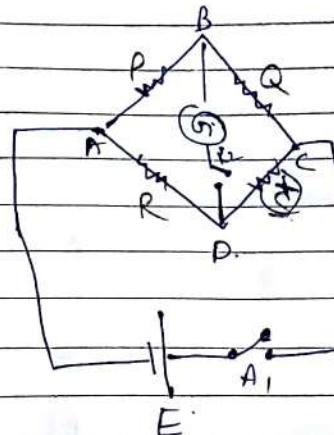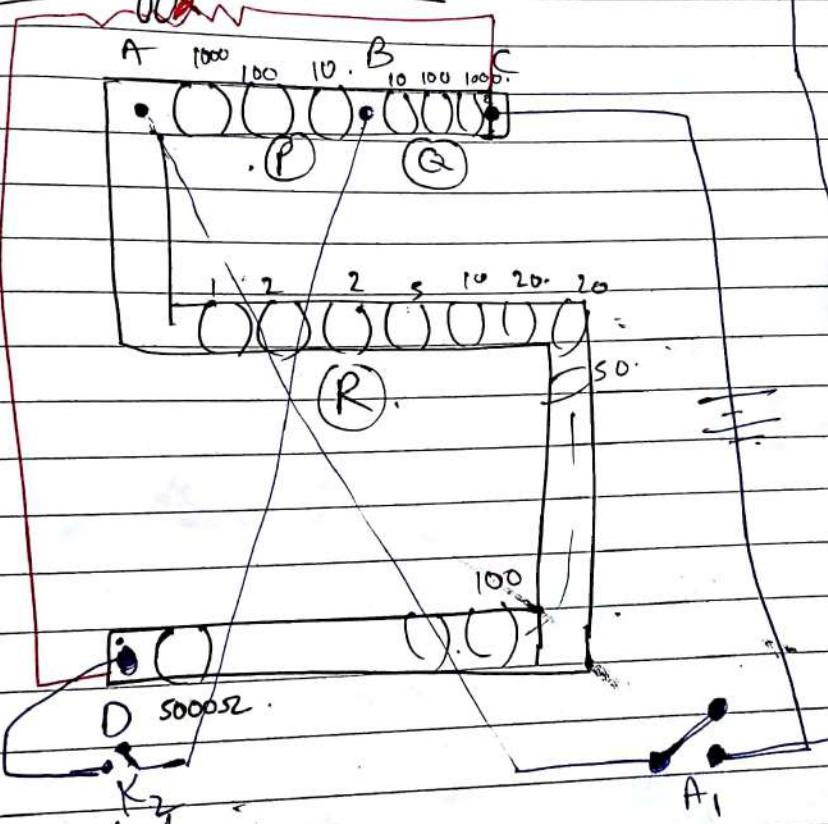

Circuit diagram

$$\underline{P = R}$$

$Q = S$

$$X = \frac{Q}{P} \cdot R$$

$$\text{by cap. } P = 10 \quad Q = 10$$

$$X = R$$

$$\Rightarrow P = 10 \quad Q = 10$$

$$X = \frac{R}{10}$$

$$R = 10X$$